 


Chapter 3. Arithmetic for Computers

Binary Addition

- Adding 6_{10} and 7_{10}

$$\begin{array}{r}
 \dots 0000\ 0000\ 0000\ 0111 \\
 + \dots 0000\ 0000\ 0000\ 0110 \\
 \hline
 \dots 0000\ 0000\ 0000\ 1101
 \end{array}$$



- Overflow in addition
 - Not possible when signs are different
 - Magnitude of result must be smaller than operands

Binary Subtraction

- Subtracting 6 from 7: $7 - 6 = 7 + (-6)$

$$\begin{array}{r} \dots 0000\ 0000\ 0000\ 0111 \\ + \dots 1111\ 1111\ 1111\ 1010 \\ \hline \dots 0000\ 0000\ 0000\ 0001 \end{array}$$

2's complement representation of -6

- No overflow if signs of both operands are the same
- Overflow possible if operands have different signs

Overflow Detection

■ Detecting overflow for 2's complement numbers

- ex) In addition, it is the overflow if sign bit becomes 1

Operation	Operand A	Operand B	Result indicating overflow
$A + B$	≥ 0	≥ 0	< 0
$A + B$	< 0	< 0	≥ 0
$A - B$	≥ 0	< 0	< 0
$A - B$	< 0	≥ 0	≥ 0

■ Overflow of Unsigned Integers

- Addition overflows if the sum is less than either of the addends
 - Overflow if $A+B=S$ and $S < A$ or $S < B$
- Subtraction overflows if the difference is greater than the minuend
 - Overflow if $A-B=S$ and $S > A$

■ How to handle overflow differs from language to language

- C, Java: ignore integer overflow
- Ada, Fortran: overflow must be notified to program


Multiplication

Steps of multiplication

$$\begin{array}{r}
 \text{multiplicand} \quad 1000_{\text{ten}} \\
 \text{multiplier} \quad \times 1001_{\text{ten}} \\
 \hline
 1000 \\
 0000 \\
 0000 \\
 1000 \\
 \hline
 \text{product} \quad 10010000_t
 \end{array}$$

Max Length of product =
length of multiplicand
+ length of multiplier

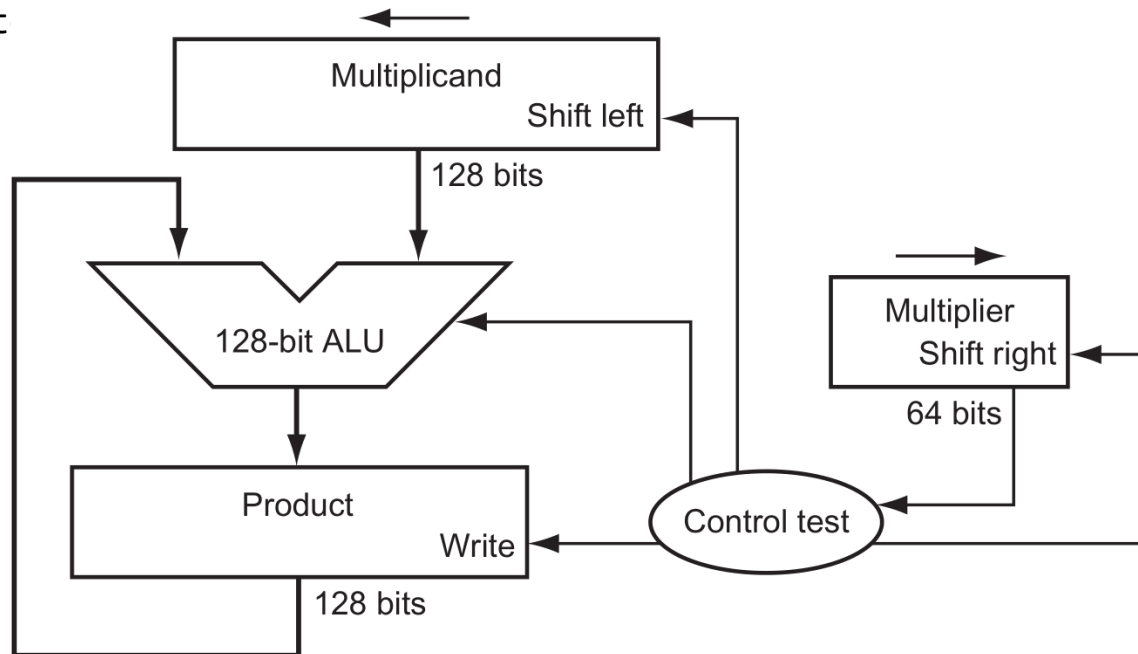- Multiplication Hardware
 - First version
 - Sequential processing




Multiplication

Initialization

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

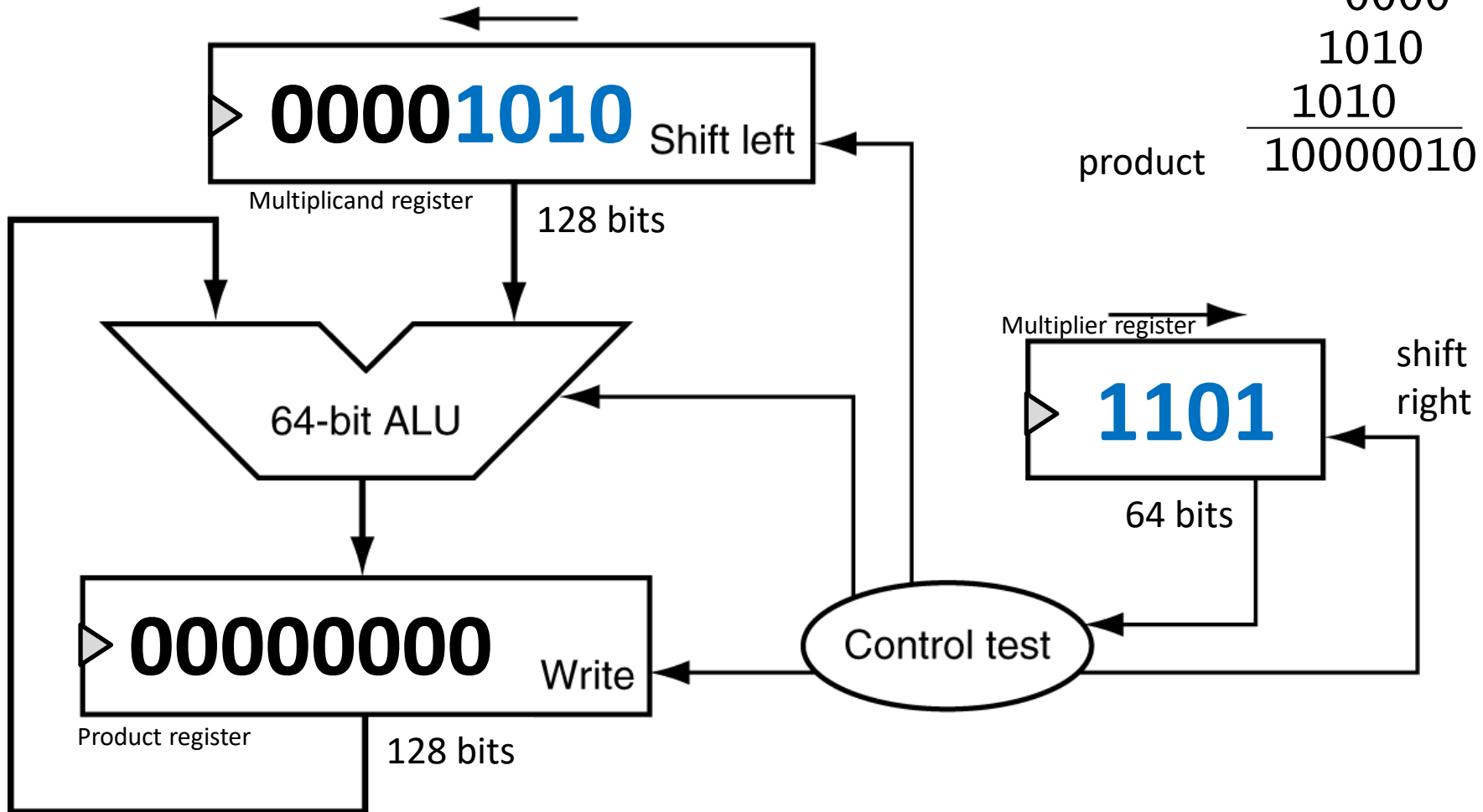


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Control signal set-up

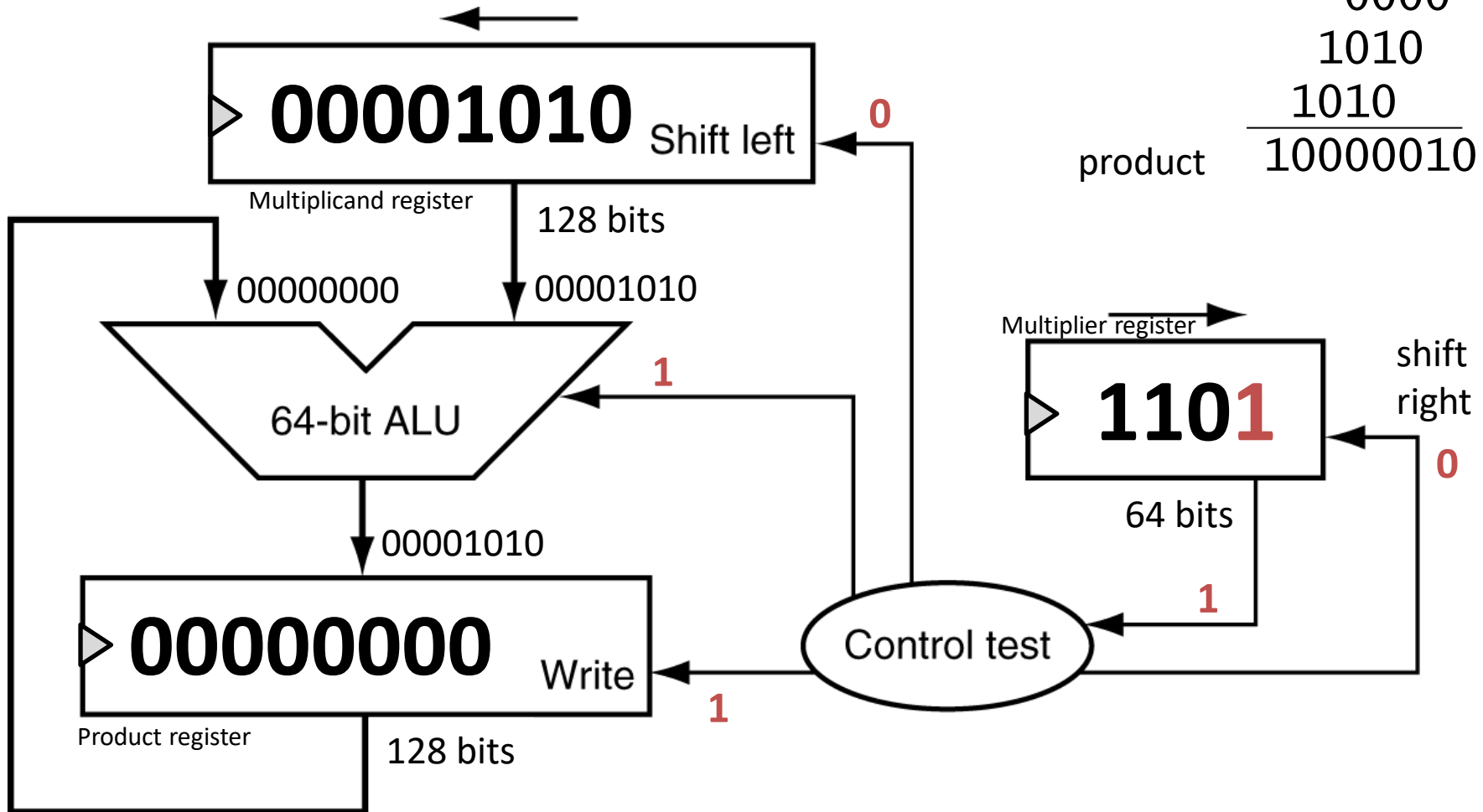


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Clock signal firing

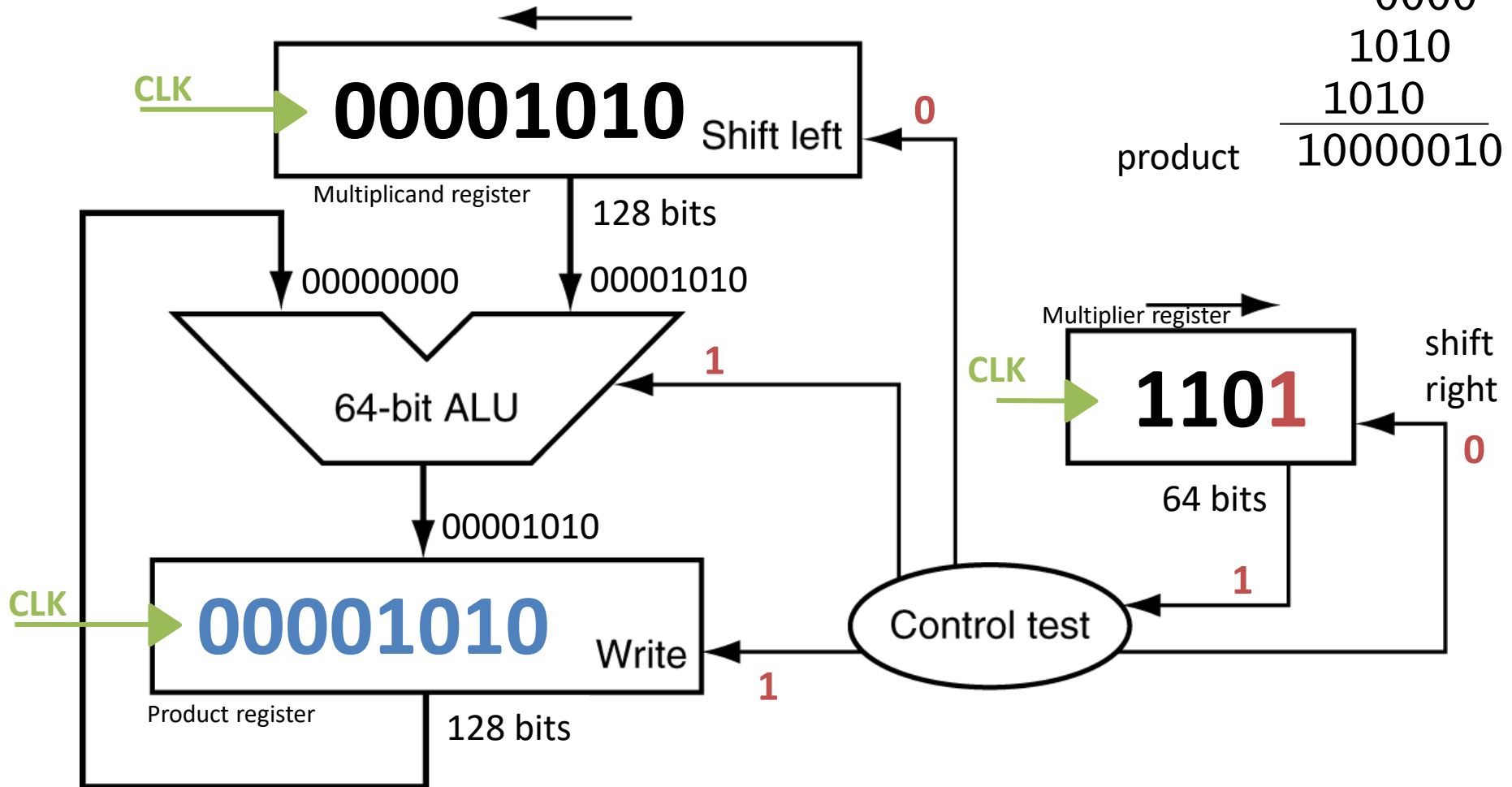


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Product register updated

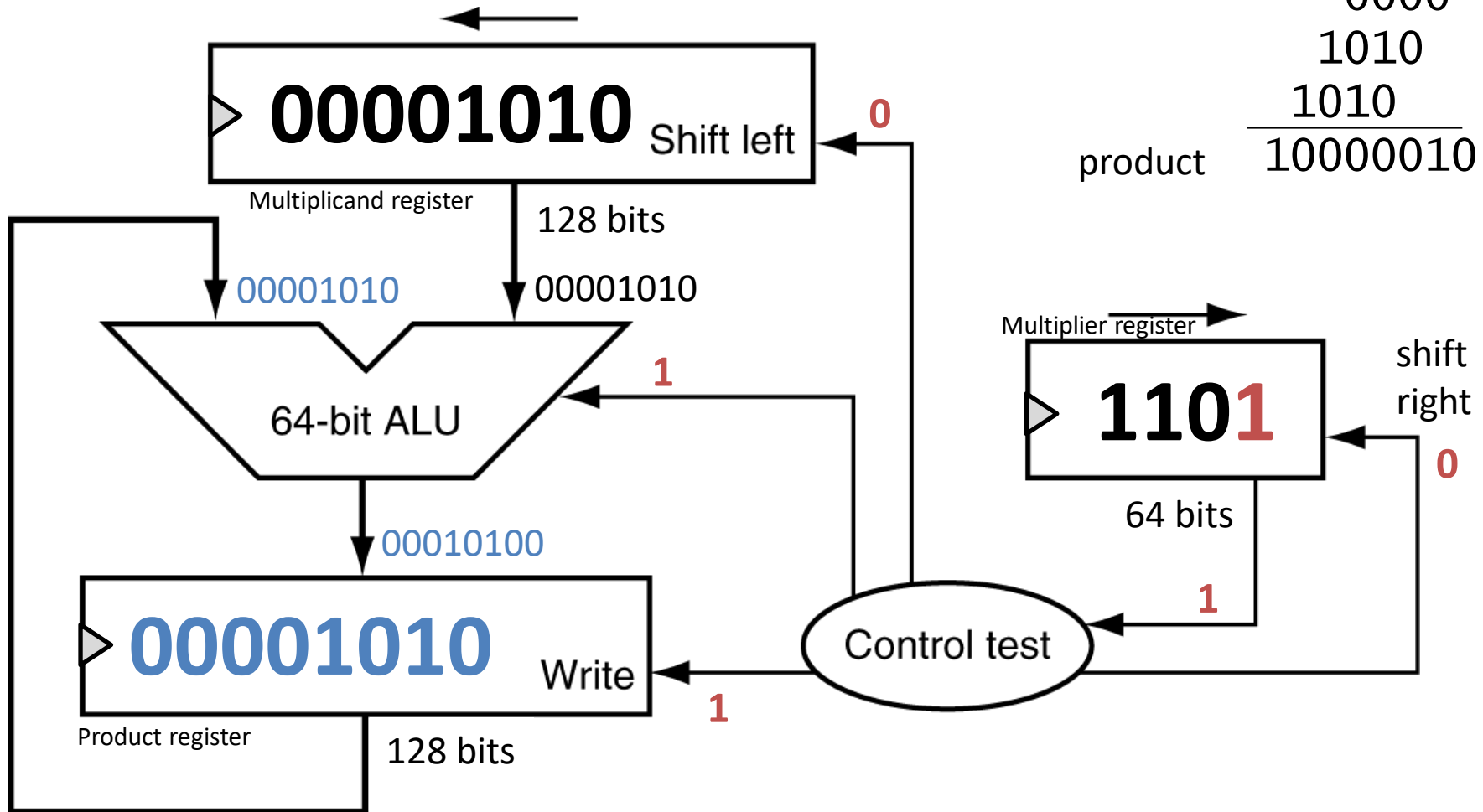


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

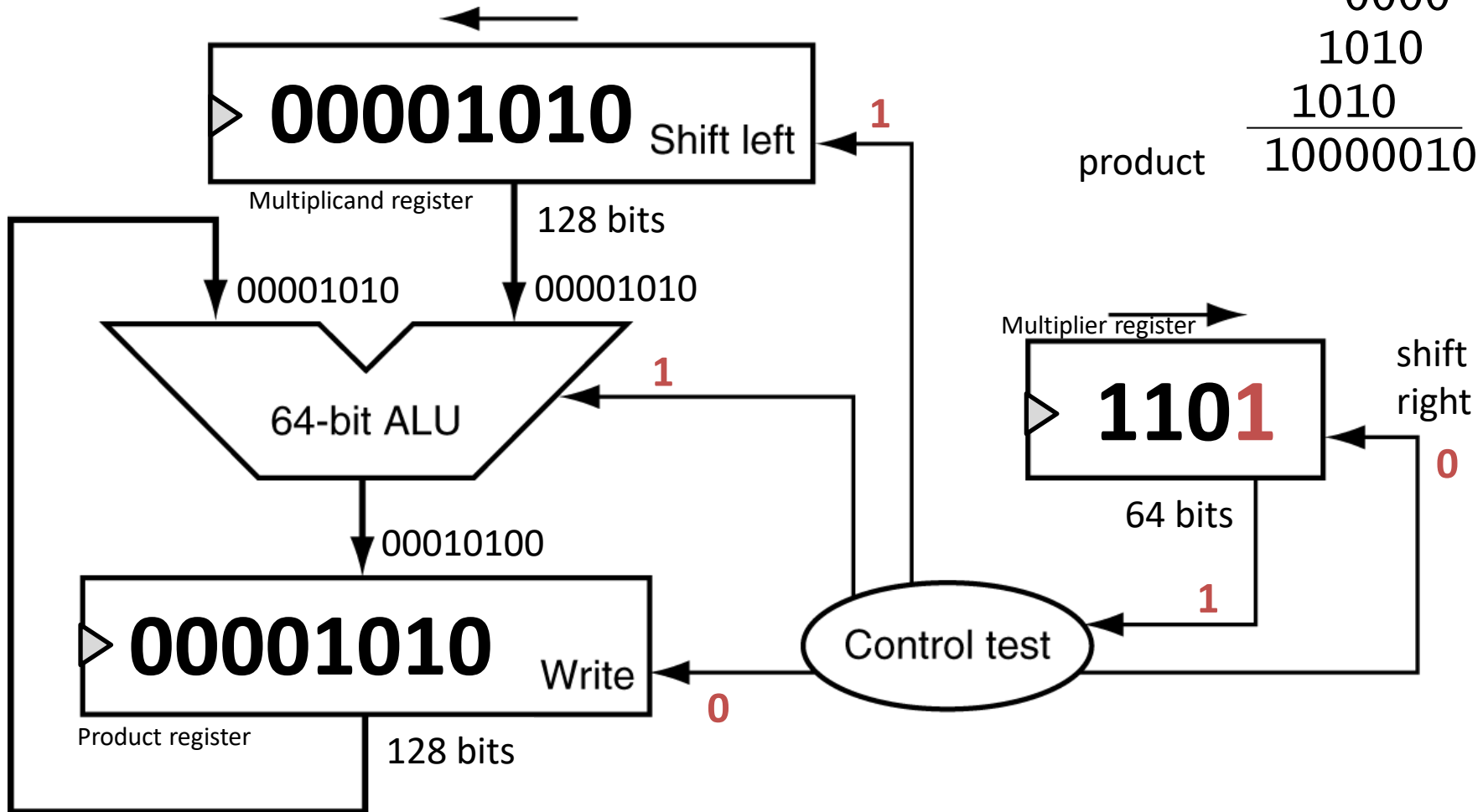Iteration 1: Control signal for shifting multiplicand




Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Clock firing

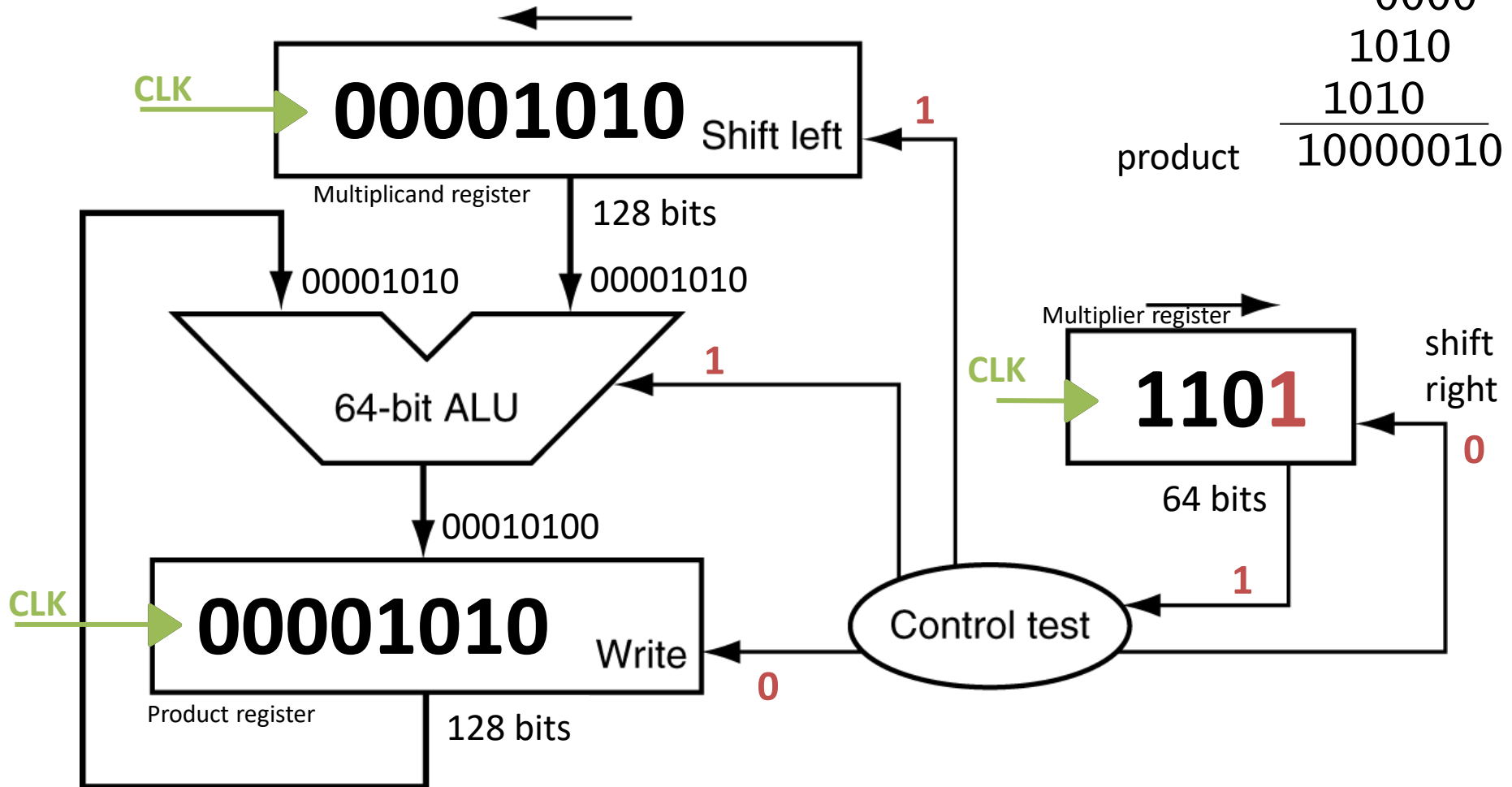


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Multiplicand shifted left

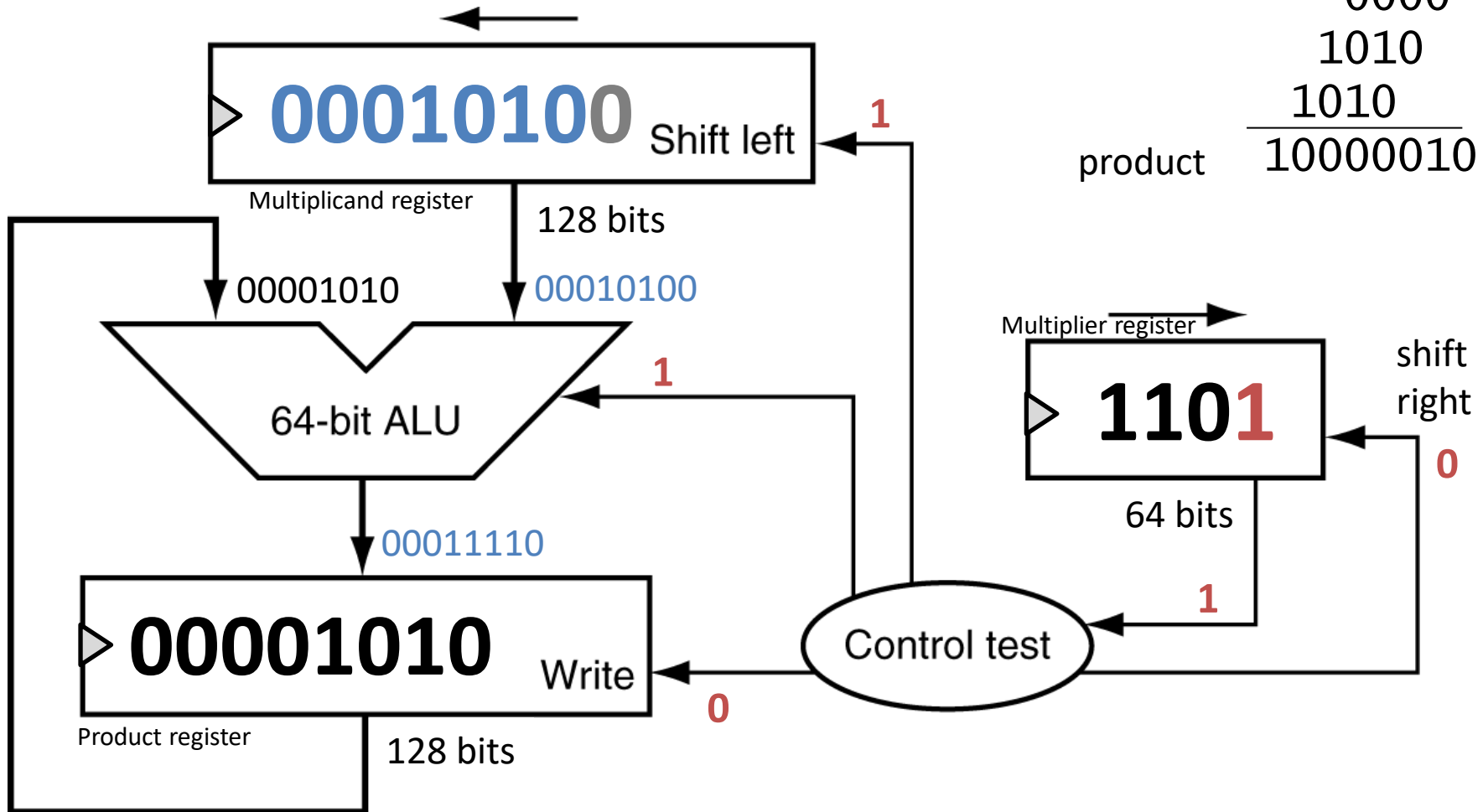


Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

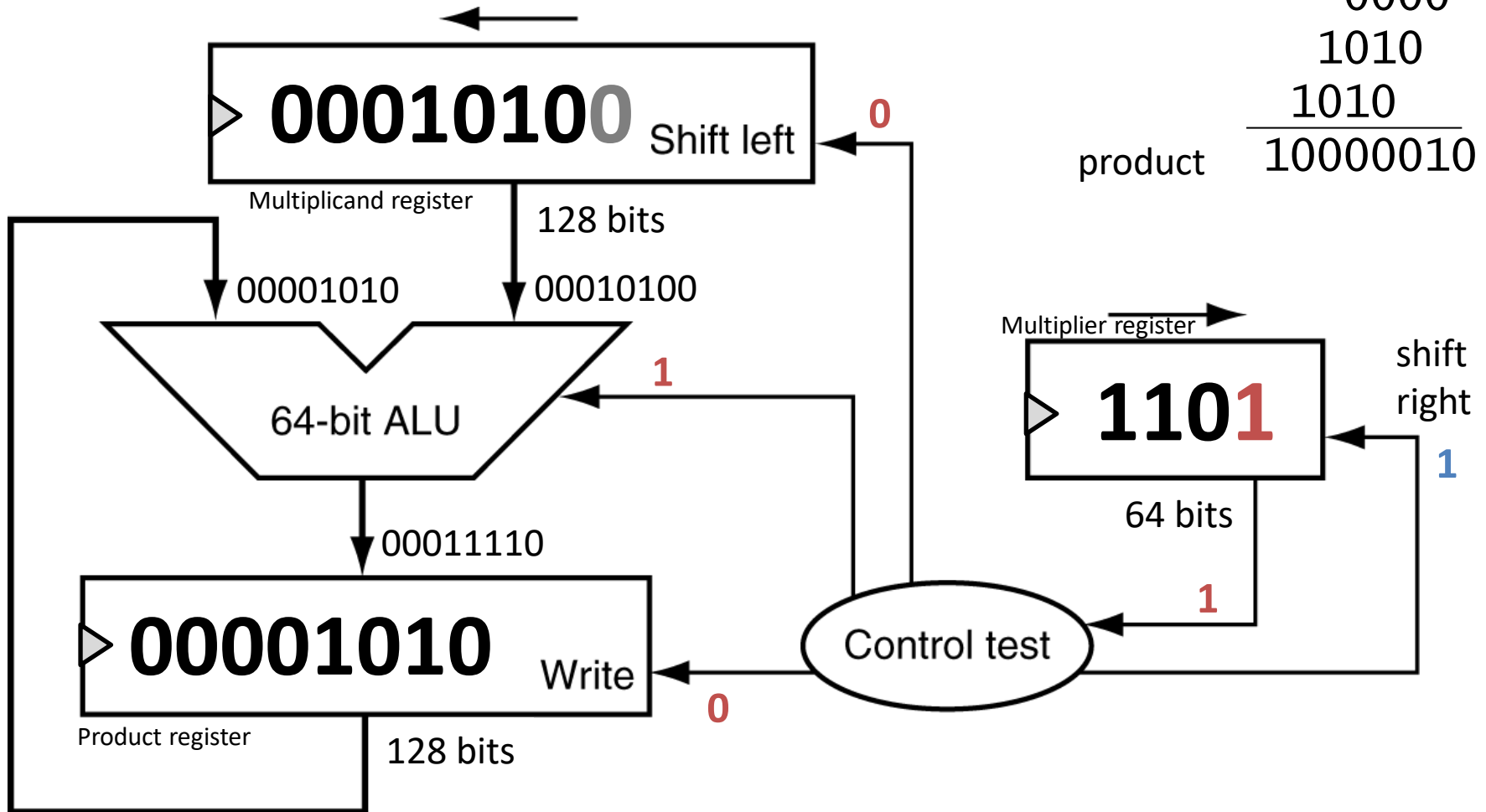Iteration 1: Control signal for shifting multiplier




Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Clock firing

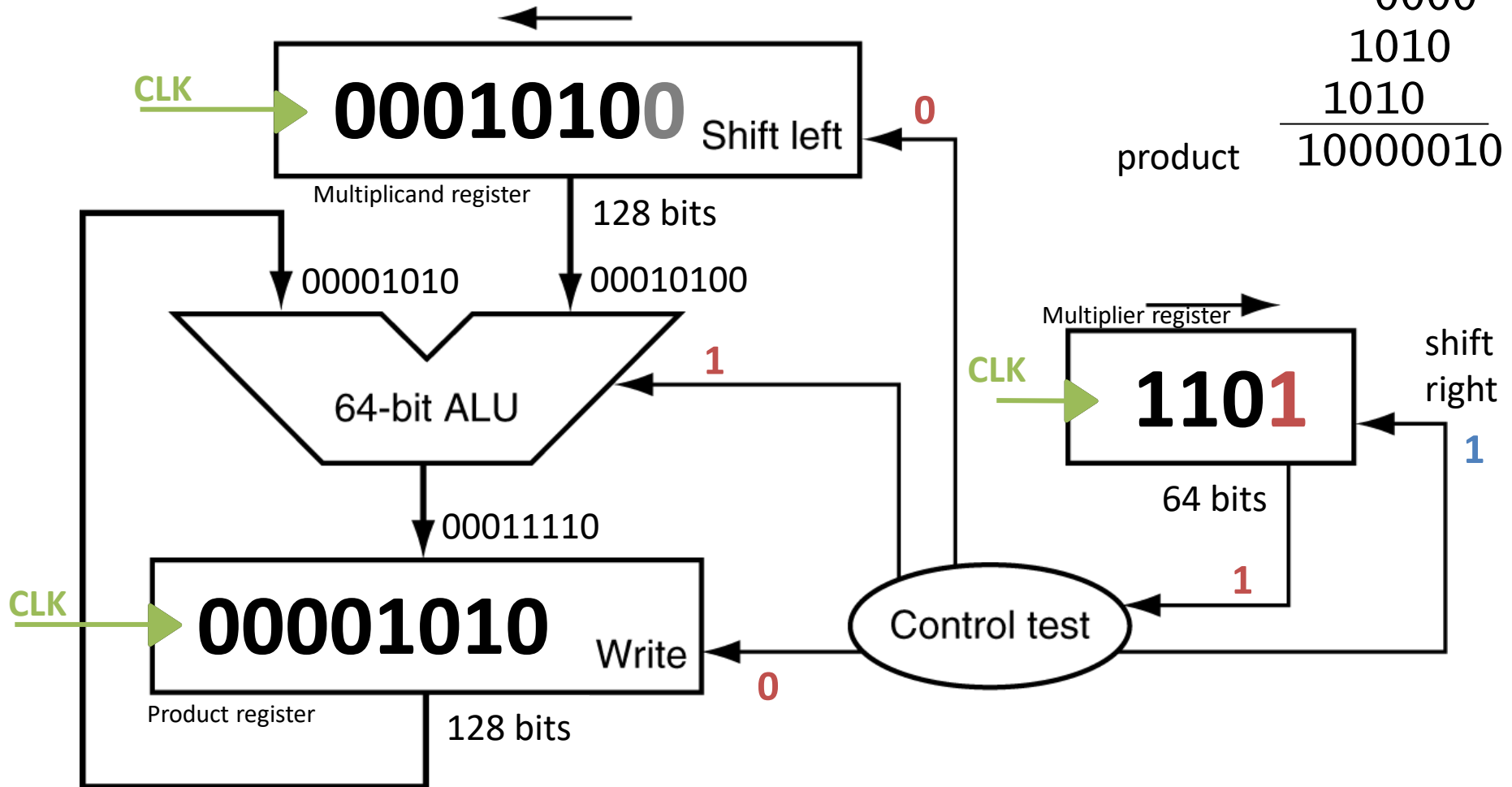


Multiplication


multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>

Iteration 1: Multiplier shifted

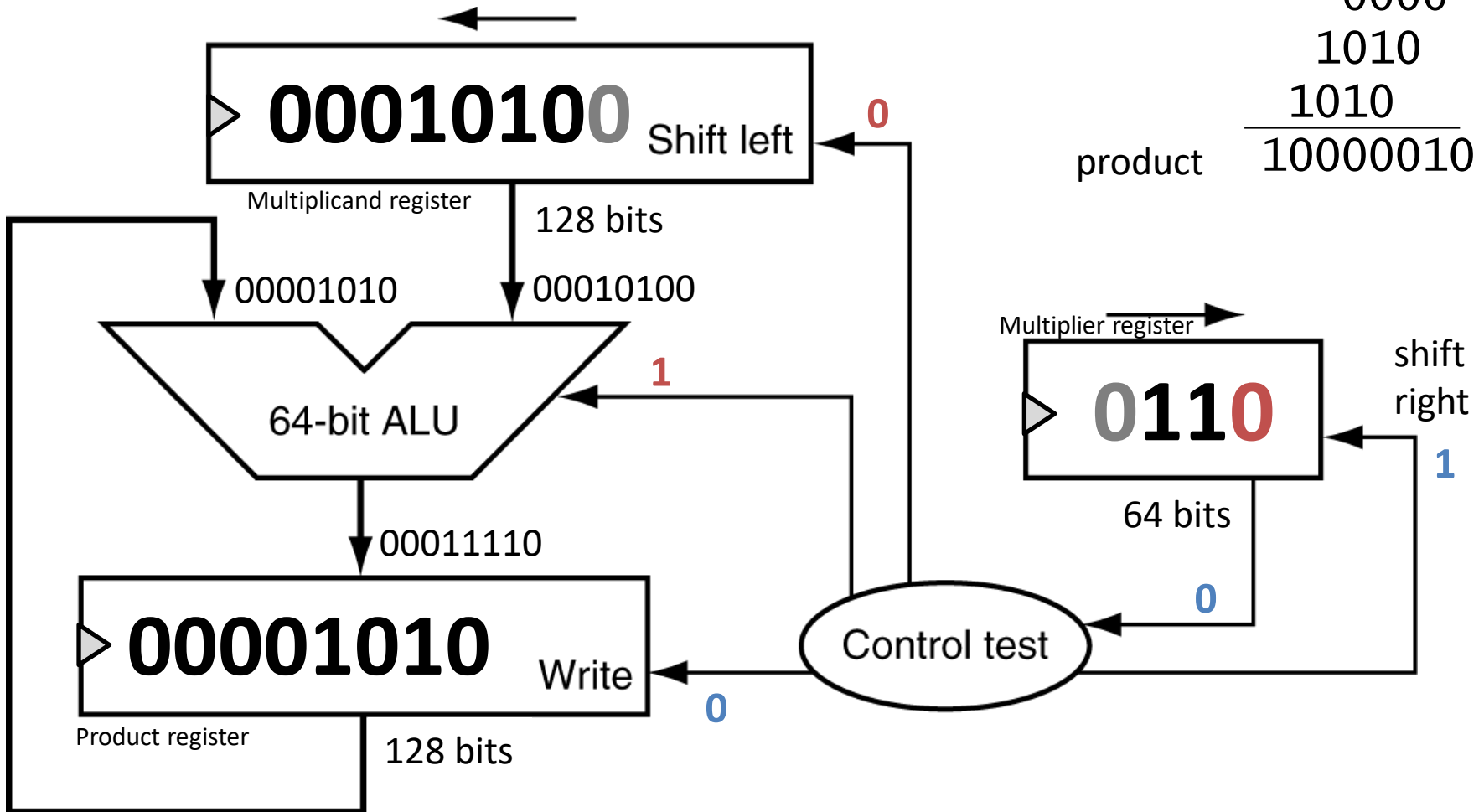

Improving the Multiplication

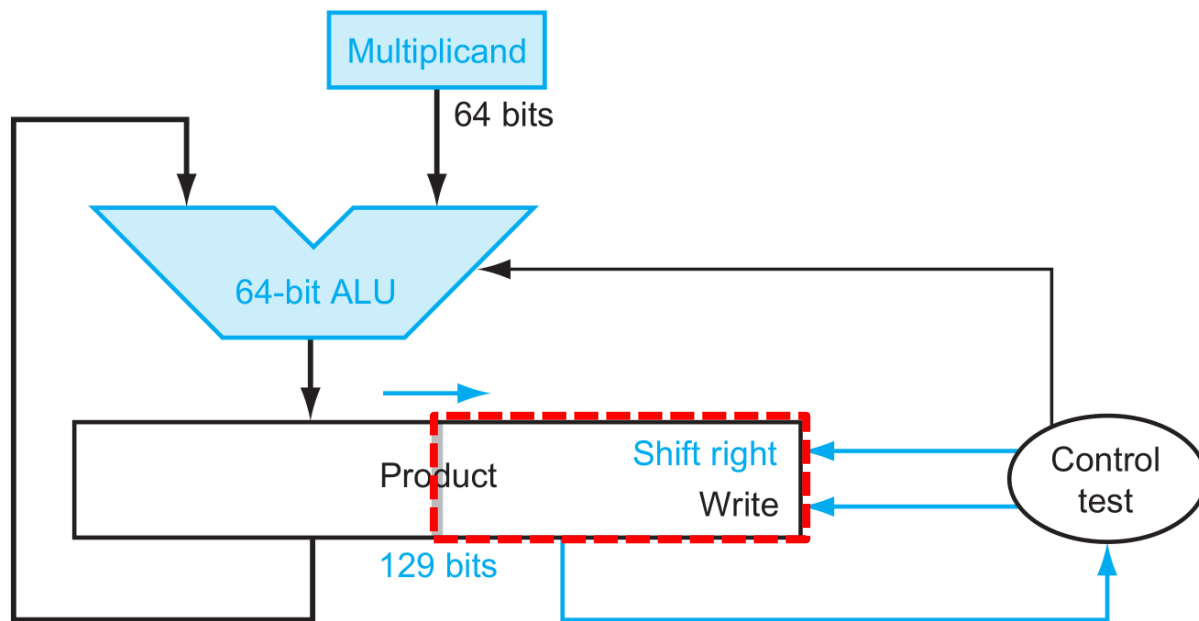


- Multiplicand register, ALU, Multiplier register are 64 bits
- Product register is 129 bits
- Multiplier placed in the right half of product register
- Addition and shifts occur in parallel

Improving the Multiplication

Initialization

multiplicand	1010
multiplier	× 1101
<hr/>	
	1010
	0000
	1010
	1010
product	<hr/> 10000010

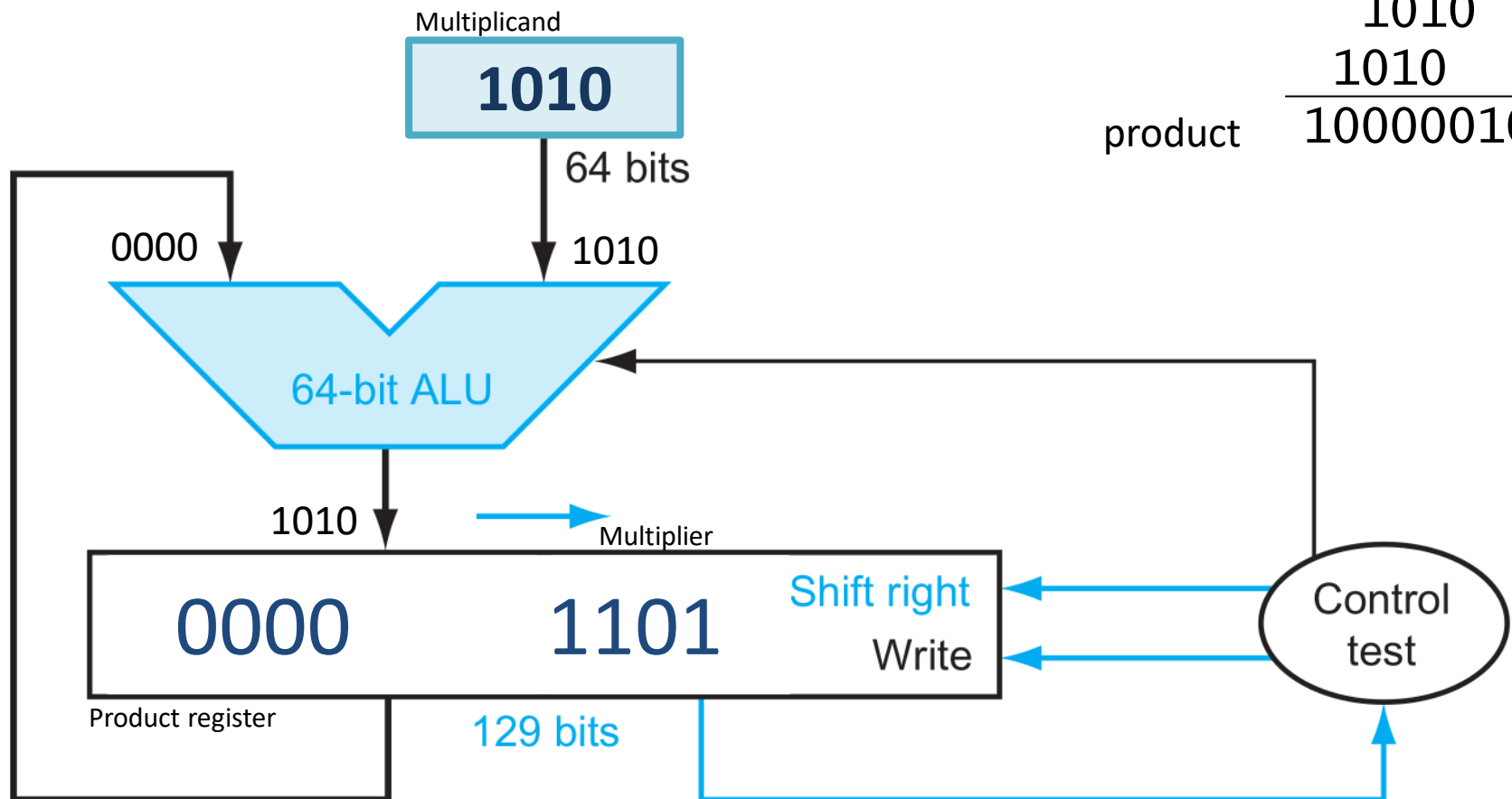


Improving the Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>


Iteration 1: Test LSB

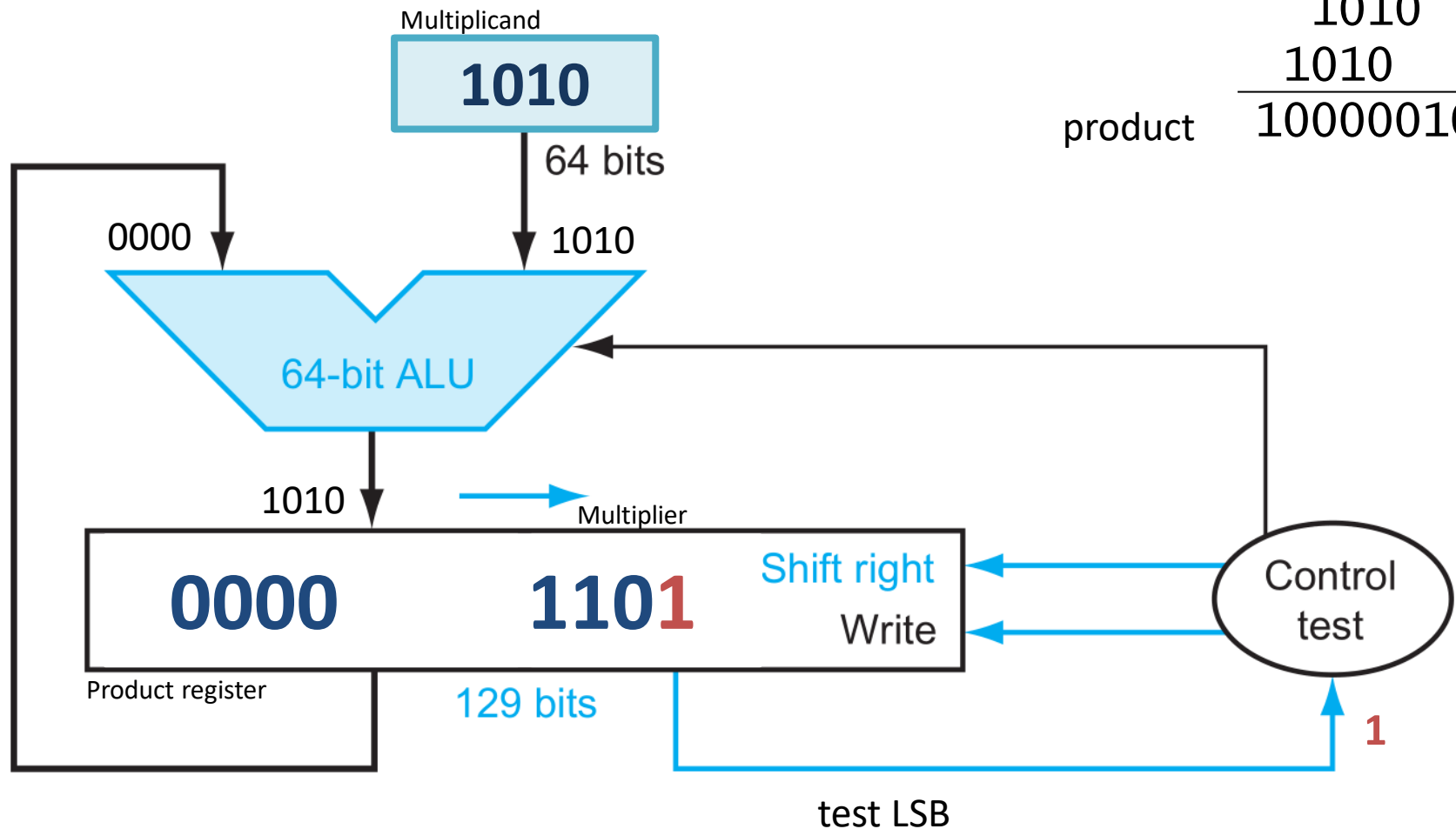

Improving the Multiplication

multiplicand	1010
multiplier	× 1101
<hr/>	
	1010
	0000
	1010
	1010
product	<hr/> 10000010


Iteration 1: Control signal setup

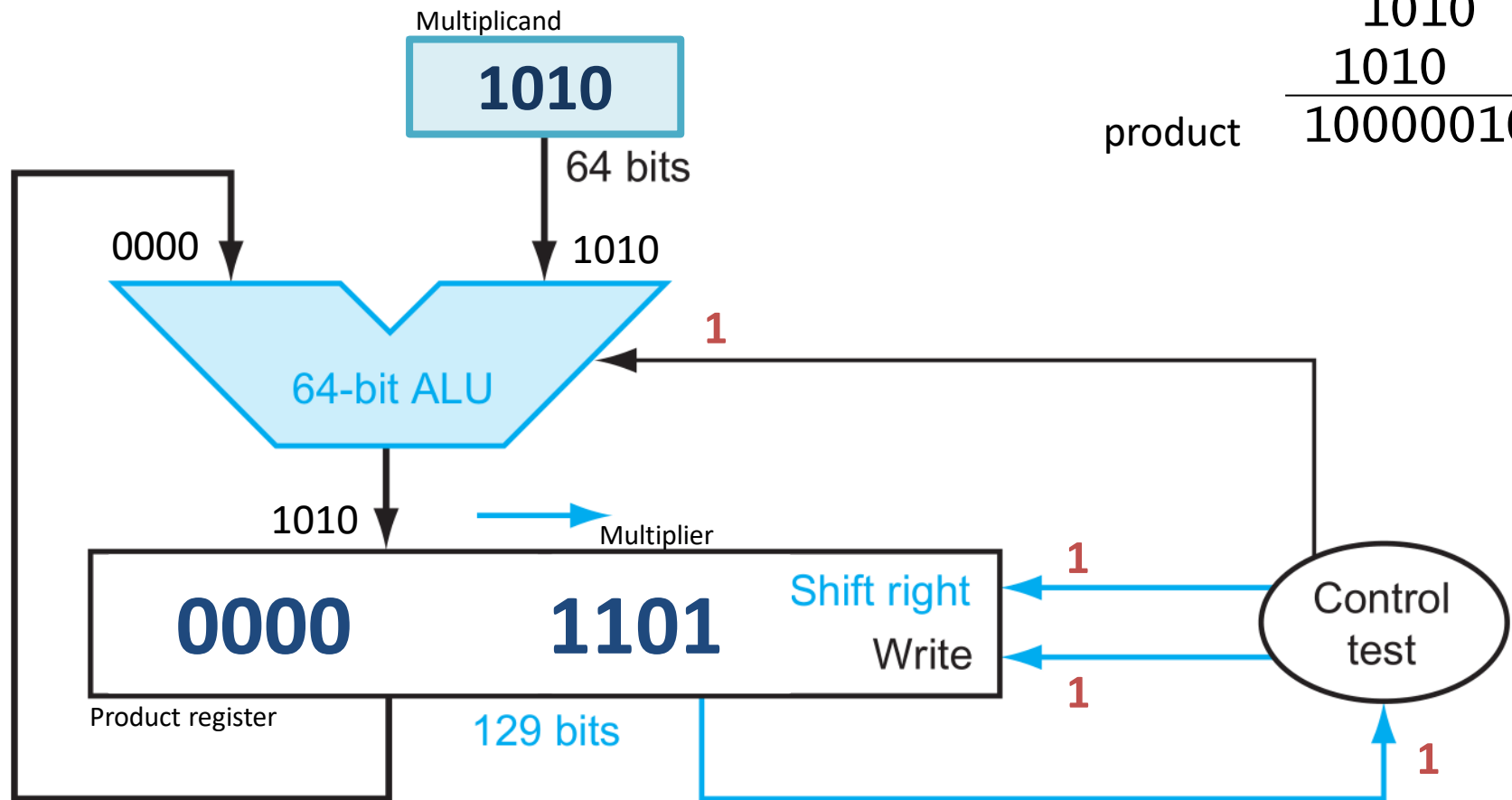

Improving the Multiplication

multiplicand	1010
multiplier	× 1101
<hr/>	
	1010
	0000
	1010
	1010
product	<hr/> 10000010

Iteration 1: Clock firing

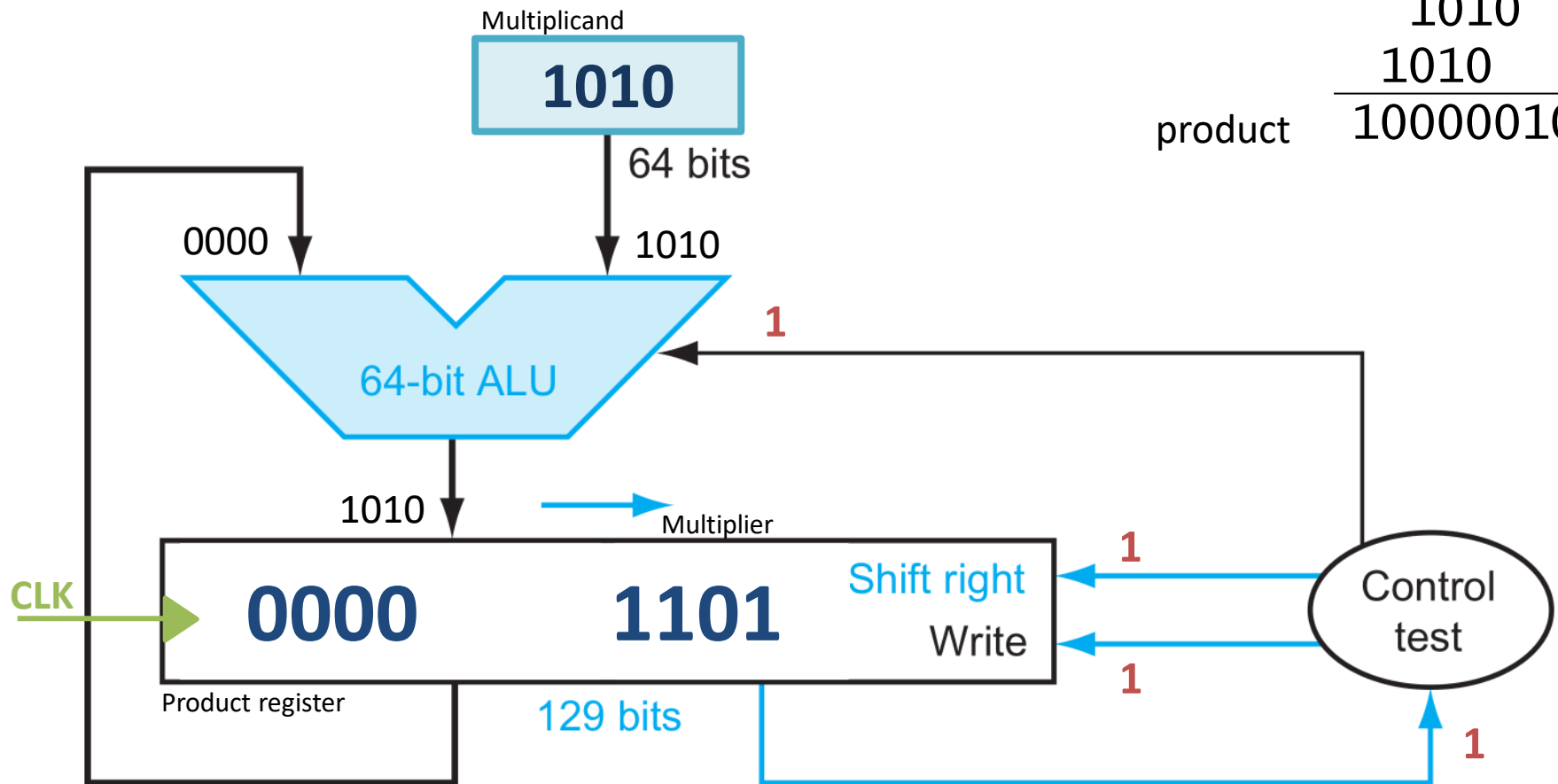


Improving the Multiplication

multiplicand	1010
multiplier	× 1101

	1010
	0000
	1010
	1010
product	<u>10000010</u>


Iteration 1: Multiplicand added

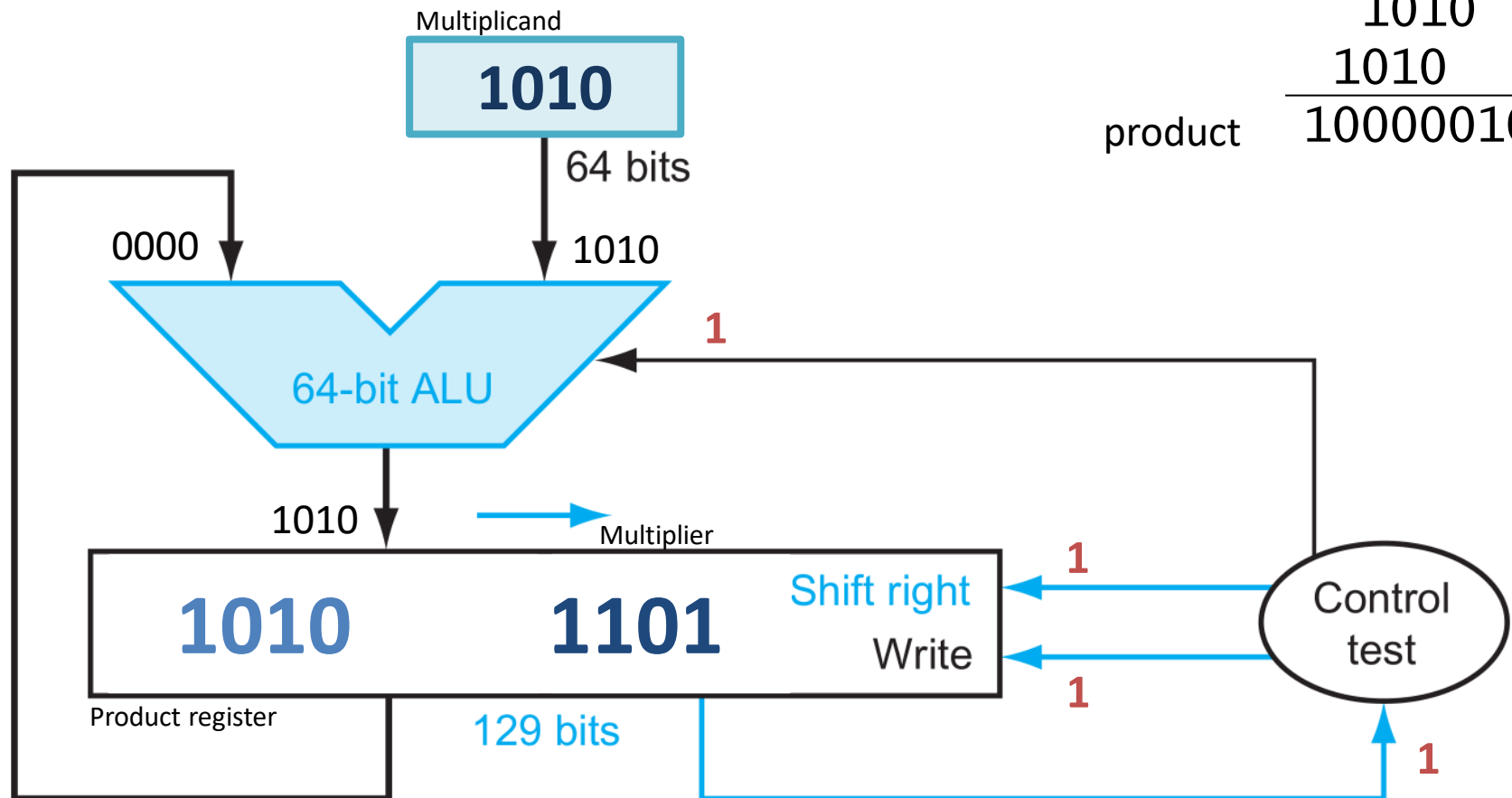

Improving the Multiplication


multiplicand	1010
multiplier	× 1101
<hr/>	
	1010
	0000
	1010
	1010
product	<hr/> 10000010

Iteration 1: Product register shifted

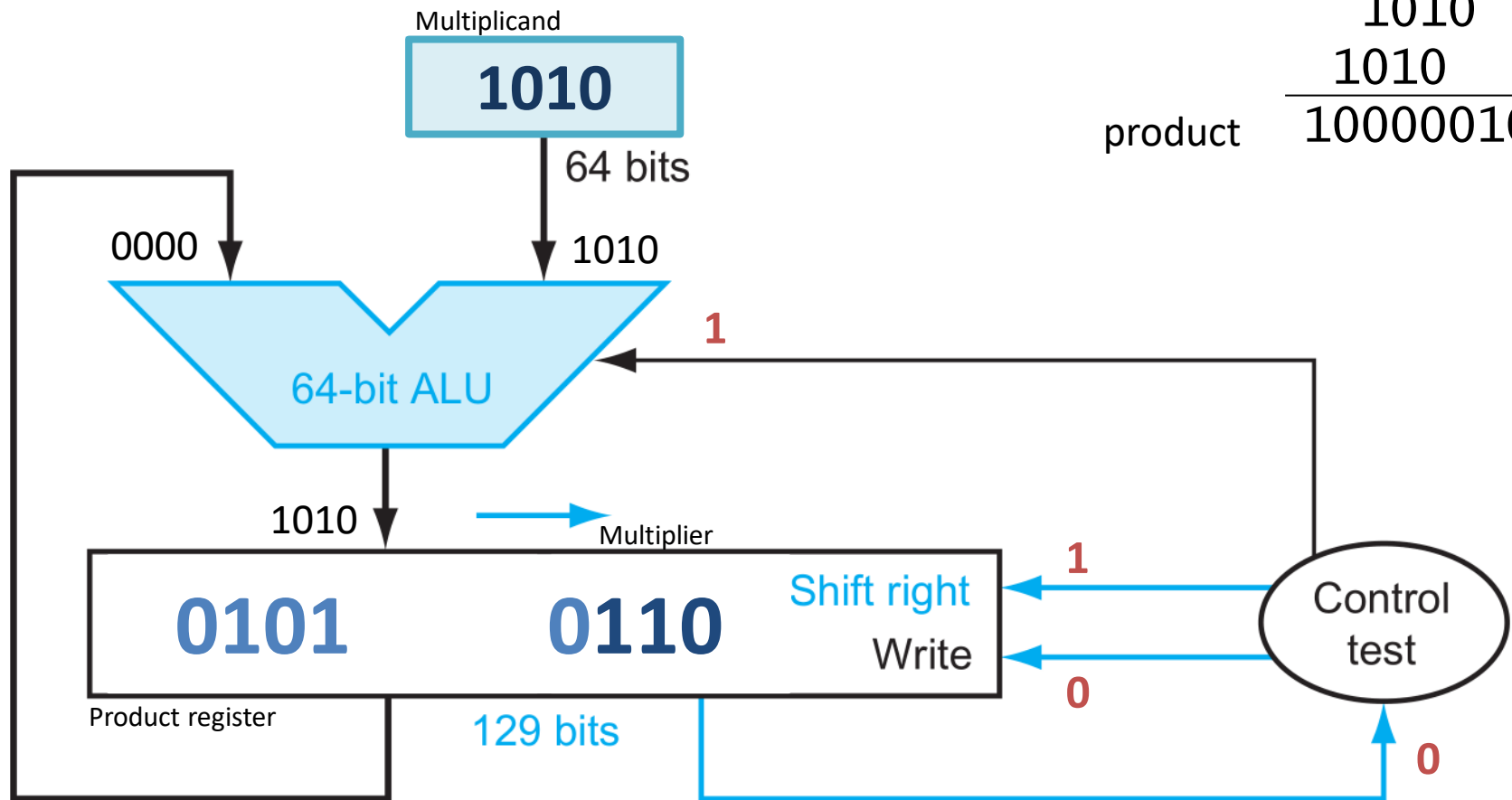

Faster Multiplication

 - Use multiple adders since multiplier is known at the beginning



- RISC-V instructions for multiplication

- Multiply: `mul rd1, rs1, rs2`
- Multiply high: `mulh rdh, rs1, rs2`
- Multiply high unsigned: `mulhu`
- Multiply high signed unsigned: `mulhsu`

```
mulhsu rdh, rs1, rs2
      signed
```

```

      10111010
    × 10001101
  -----
0000000010111010
0000000000000000
0000001011101000
0000010111010000
0000000000000000
0000000000000000
0000000000000000
0101110100000000
-----
0110011001110010
```

Division

Divisor	1000)	1001010	Quotient	1001
	-1000			Dividend	
			10		
			101		
			1010		
	-1000				
			10	Remainder	


Dividend = Quotient x Divisor + Remainder

■ Algorithm

- Subtract Divisor from Dividend (=remainder)
 - Result goes into remainder register
- If remainder ≥ 0 , write 1 to quotient
- If remainder < 0 , restore by adding divisor to remainder. Write 0 to quotient.
- Shift divisor right by 1 bit position
- Repeat this 33 times.

Division Hardware

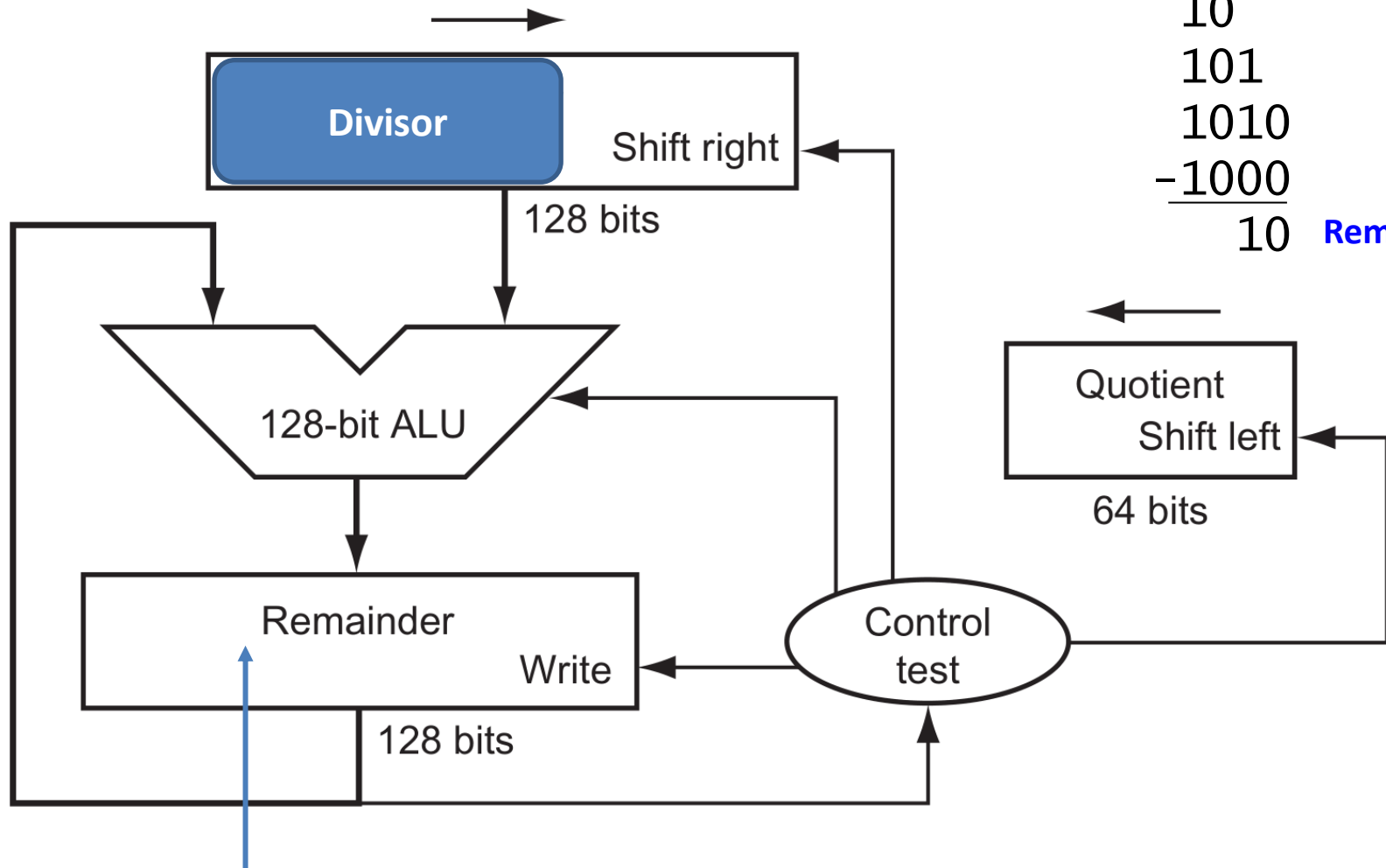Divisor 1000 $\overline{)1001010}$ **Quotient** 1001
Dividend 1001010
 $\underline{-1000}$
 10
 101
 1010
 $\underline{-1000}$
 10 **Remainder**




Dividend is place here

Division Hardware

Initialization


0111 ÷ 0010
(7 ÷ 2)

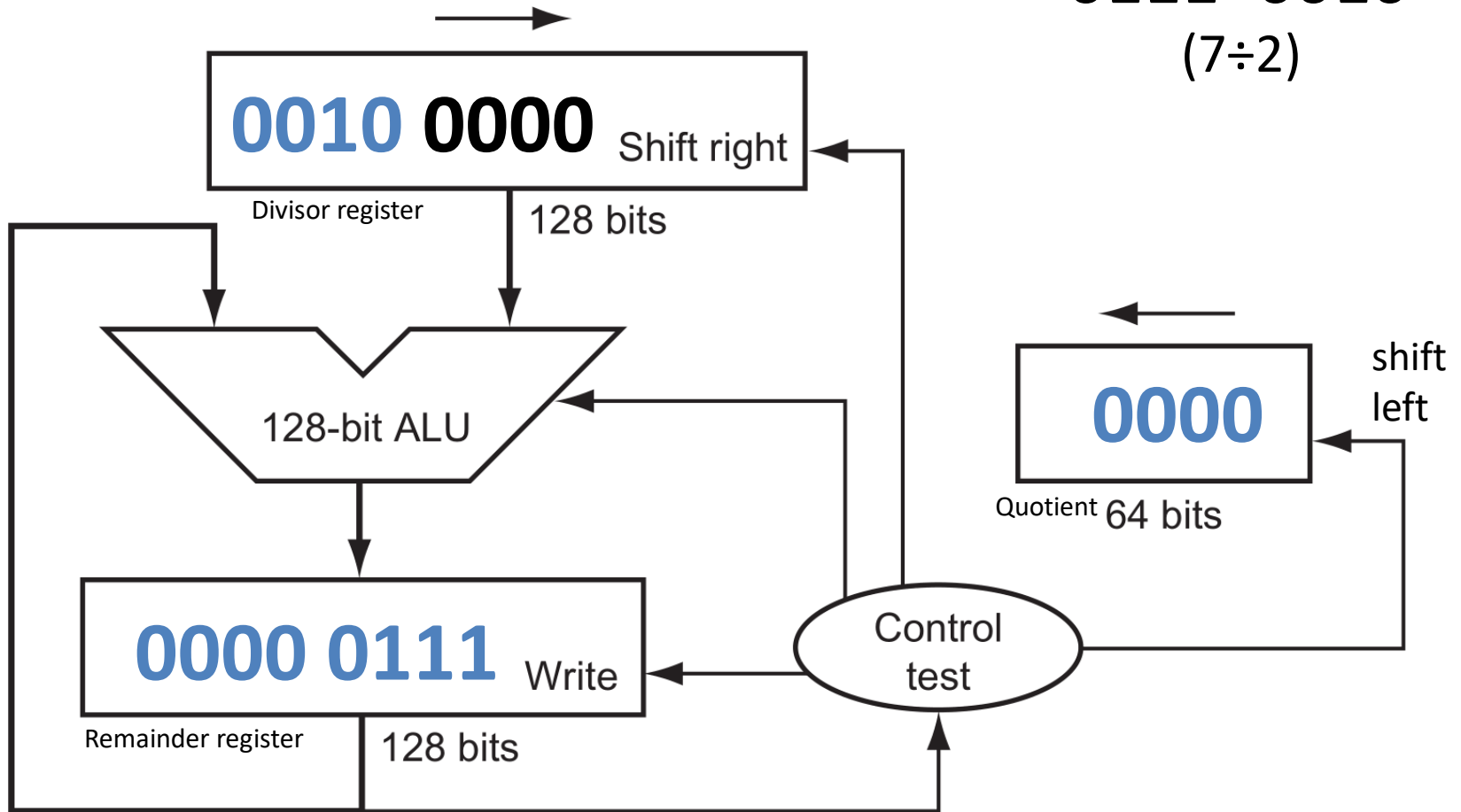

Division Hardware

Iteration 1: Control signal set-up


0111 ÷ 0010
(7 ÷ 2)

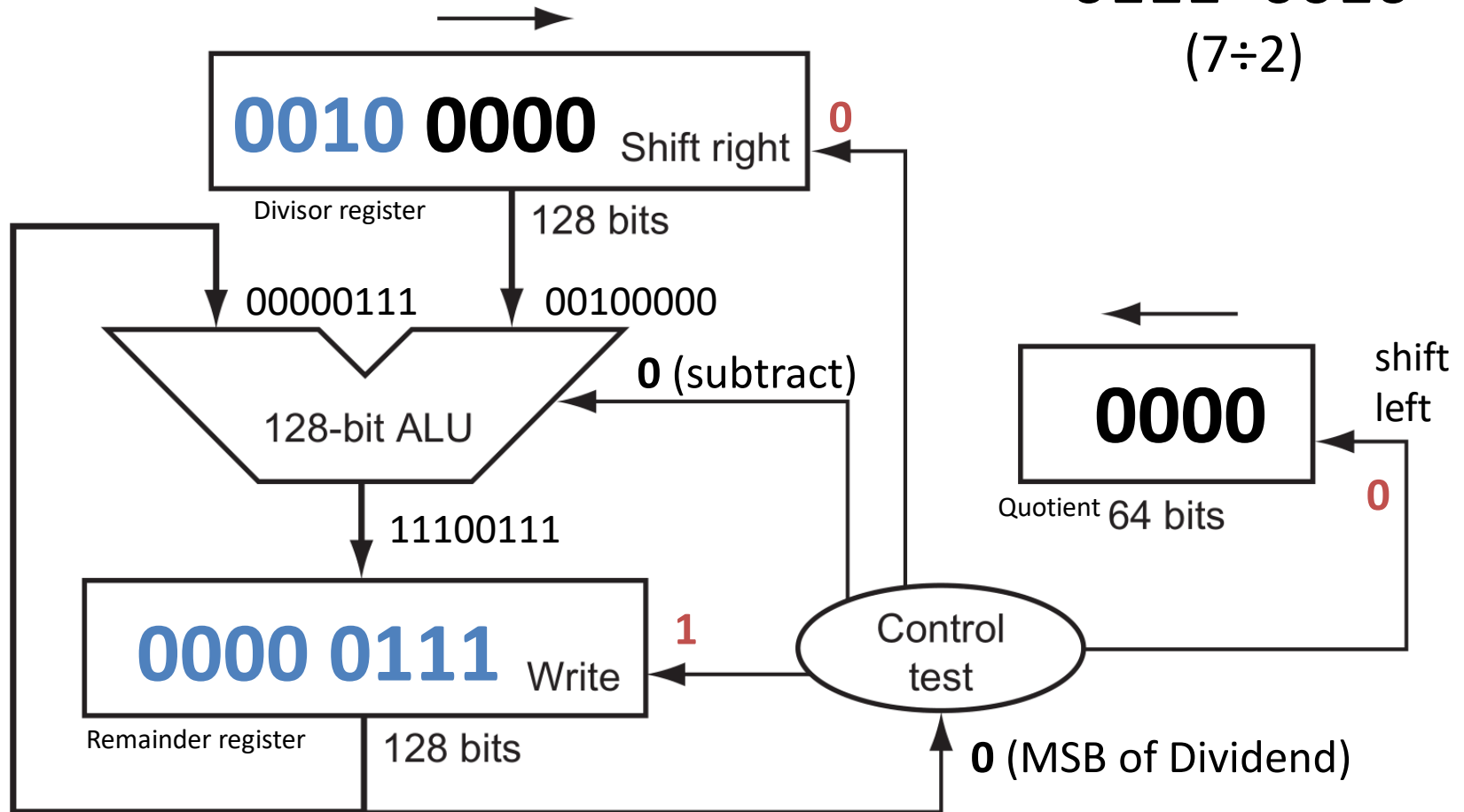

Division Hardware

Iteration 1: Clock firing (& Remainder updated)


0111 ÷ 0010
(7 ÷ 2)

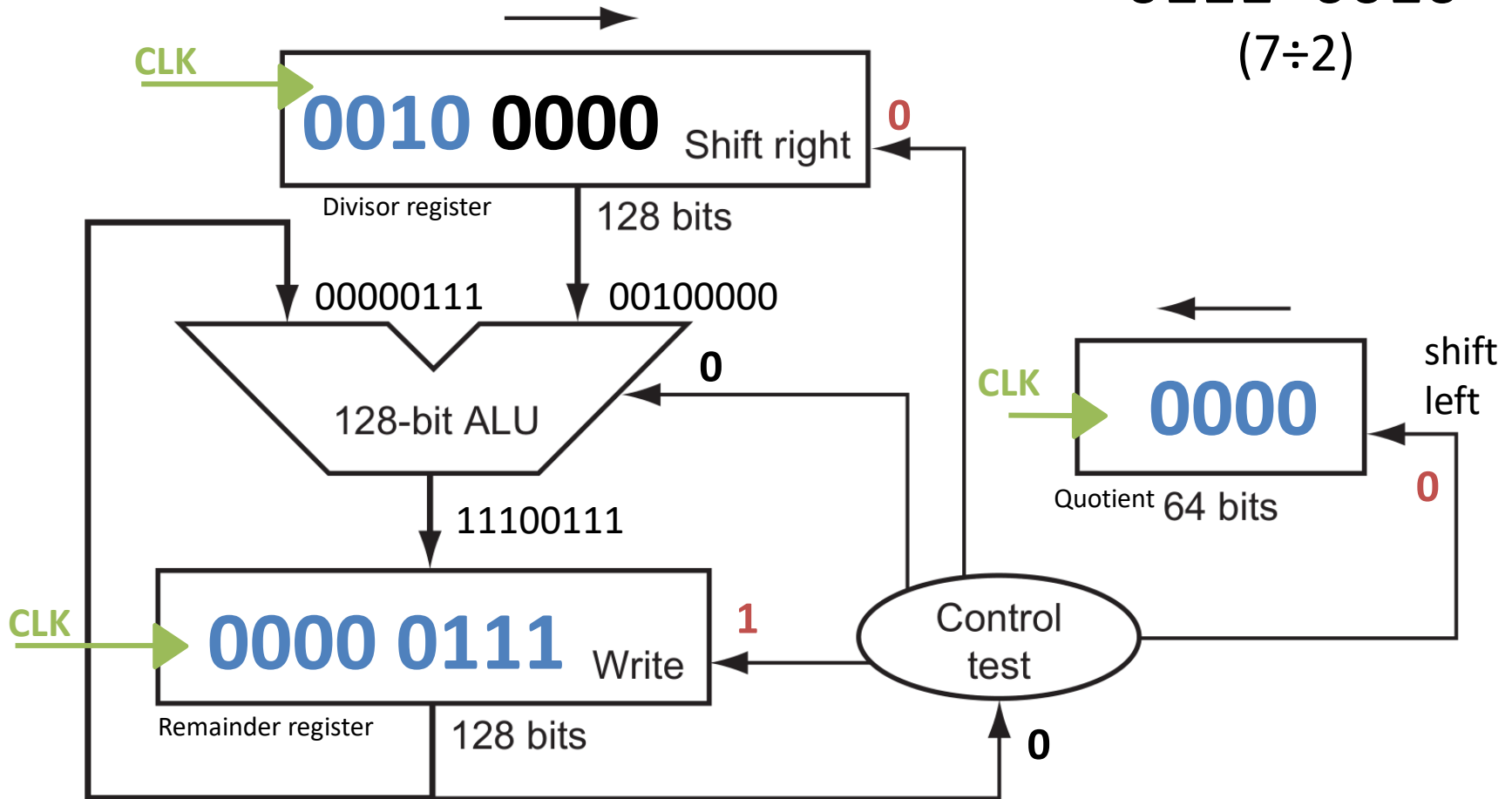

Division Hardware

Iteration 1: Test MSB of remainder


0111 ÷ 0010
(7 ÷ 2)

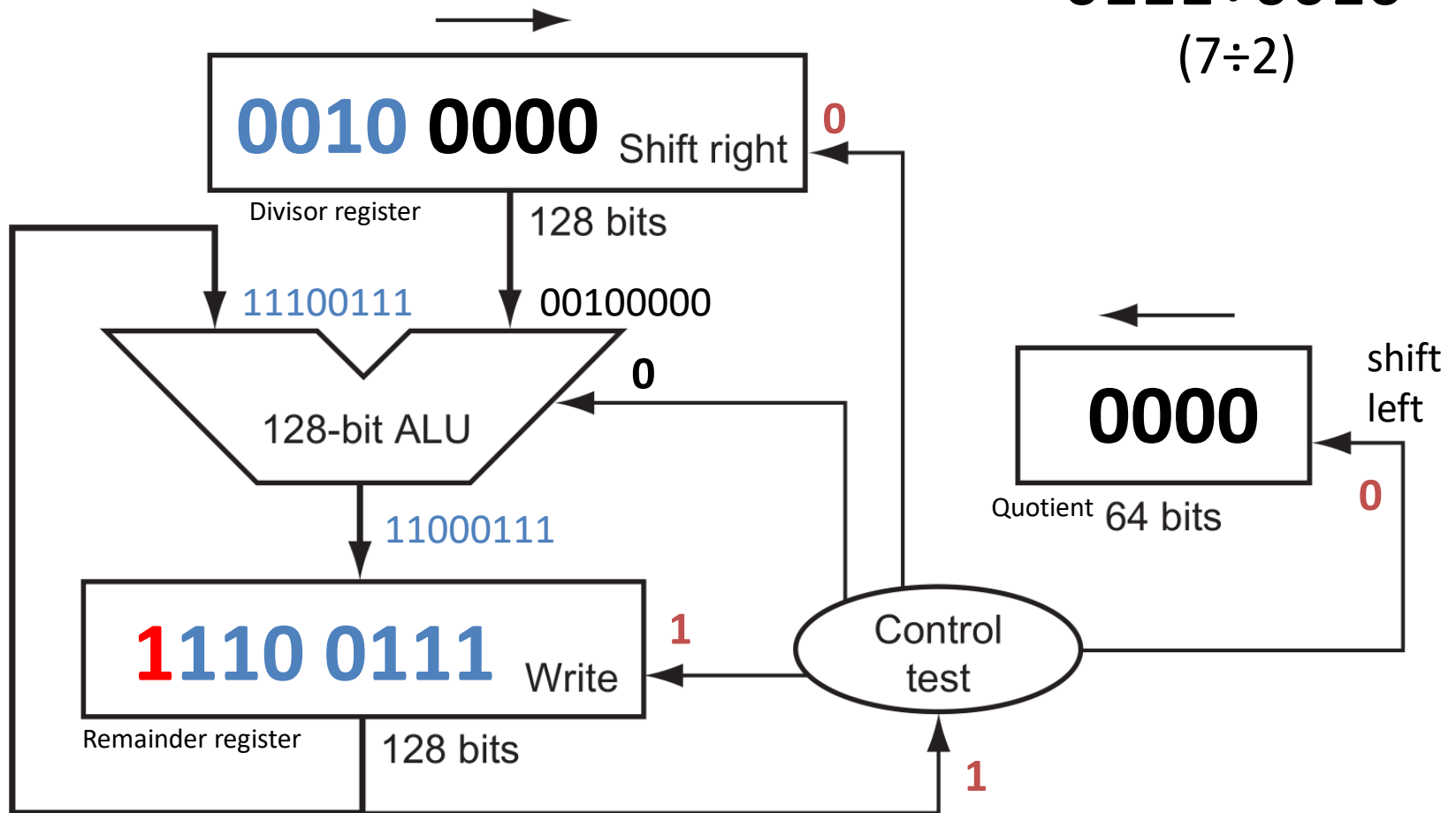

Division Hardware

Iteration 1: Control signal for ALU addition ready


0111 ÷ 0010
(7 ÷ 2)

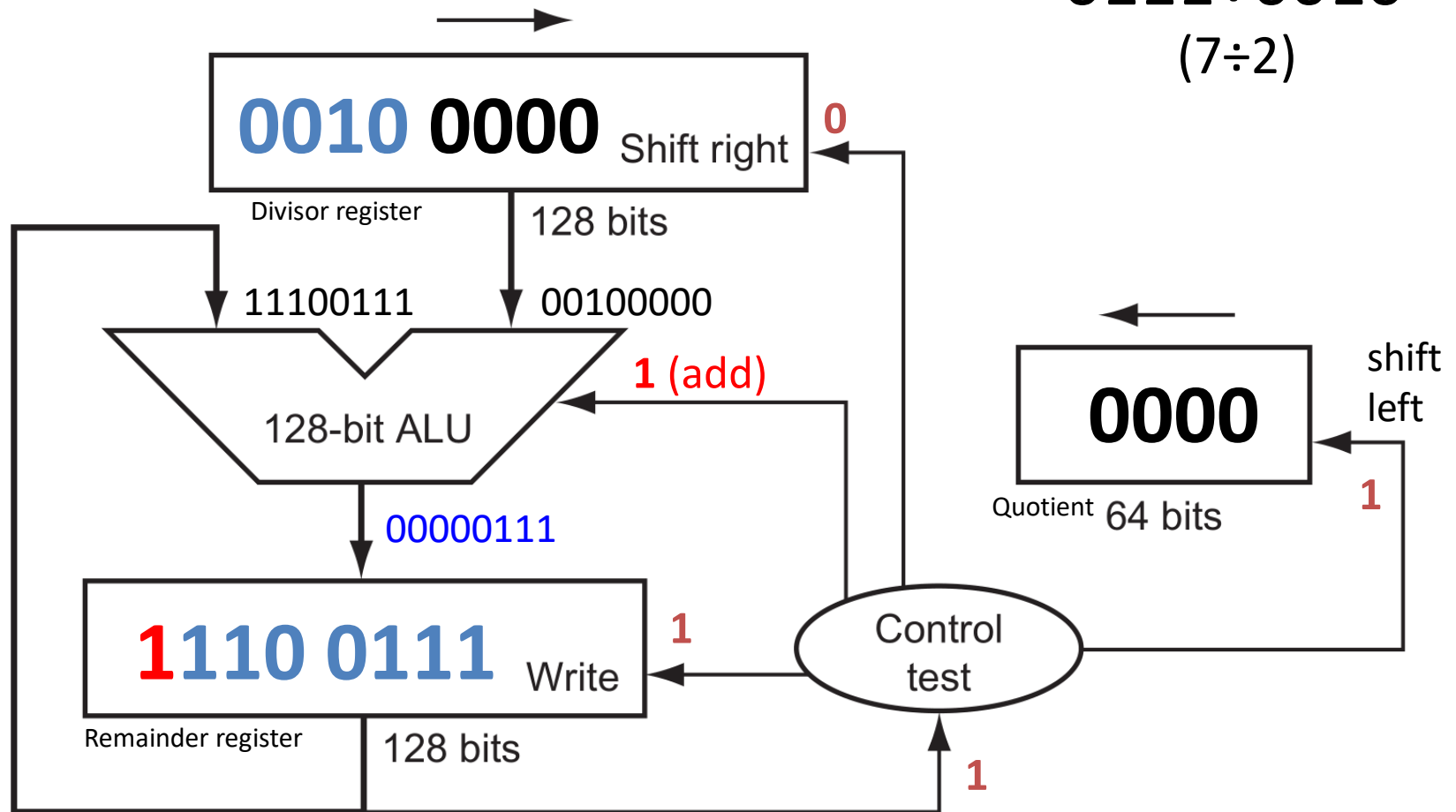

Division Hardware

Iteration 1: Clock firing (& Remainder restored)


0111 ÷ 0010
(7 ÷ 2)

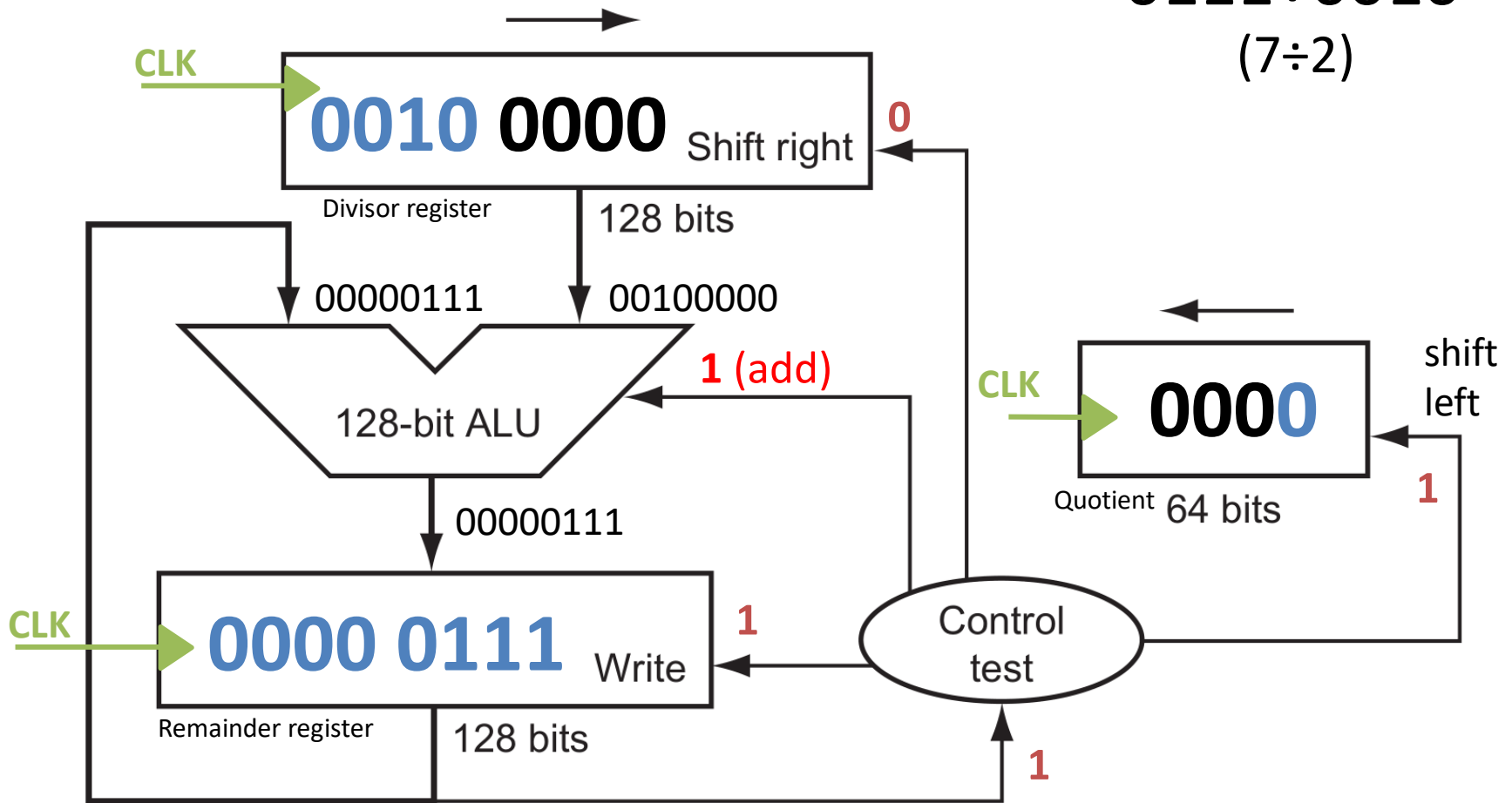

Division Hardware

Iteration 1: Control signal for divisor shift ready


0111 ÷ 0010
(7 ÷ 2)

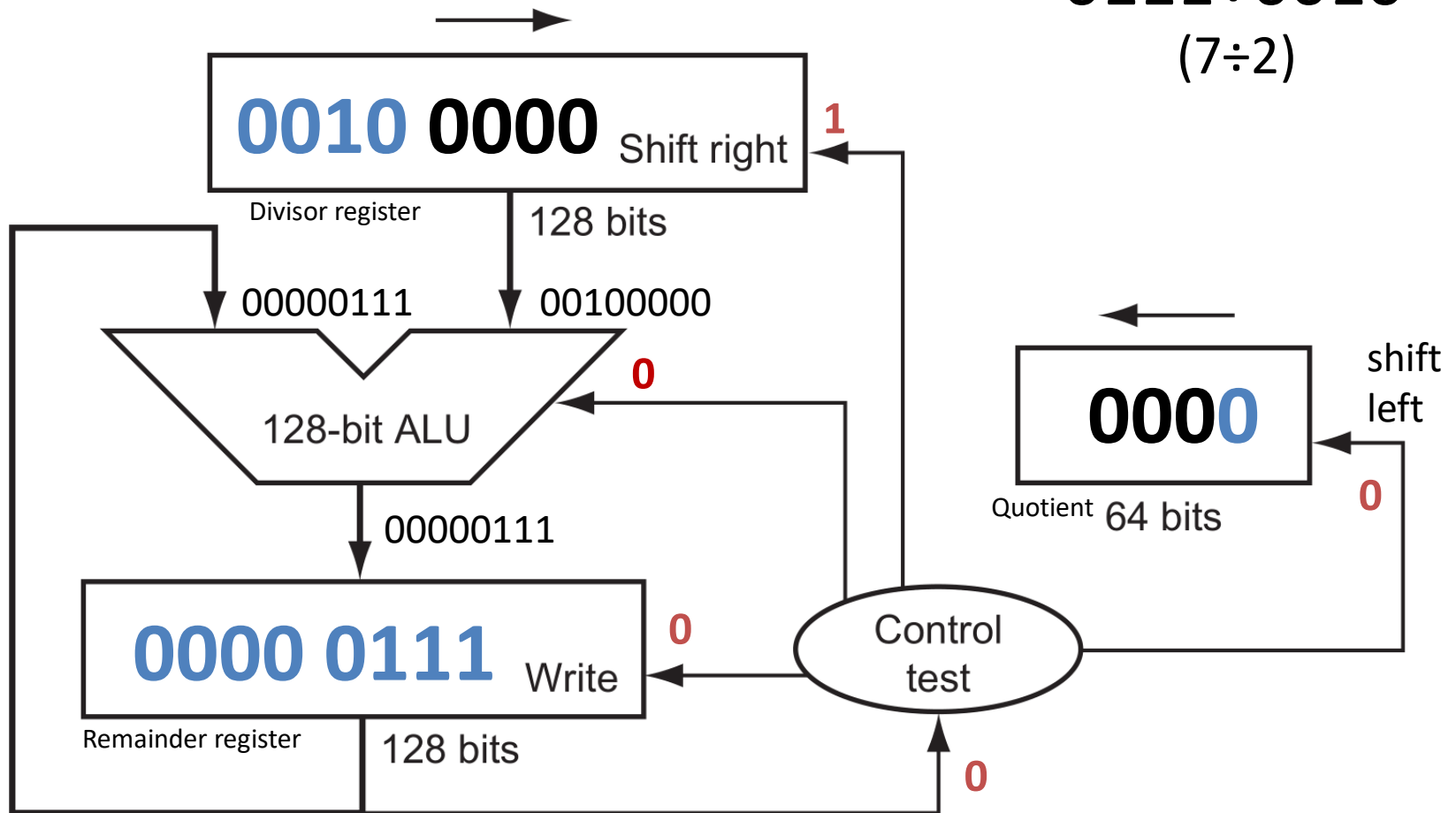

Division Hardware

Iteration 1: Clock firing


0111 ÷ 0010
(7 ÷ 2)

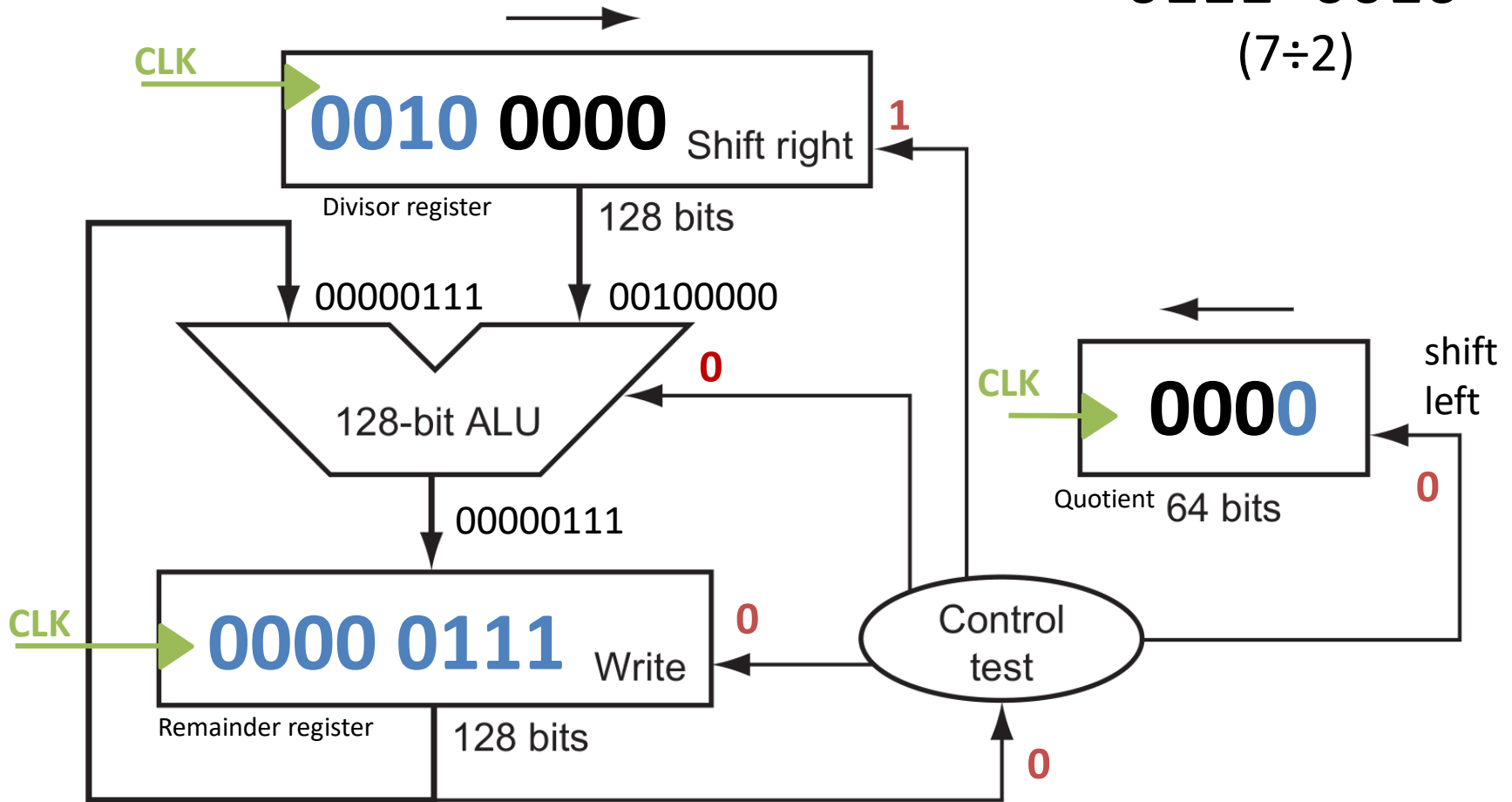

Division Hardware

Iteration 1: Divisor shifted


0111 ÷ 0010
(7 ÷ 2)

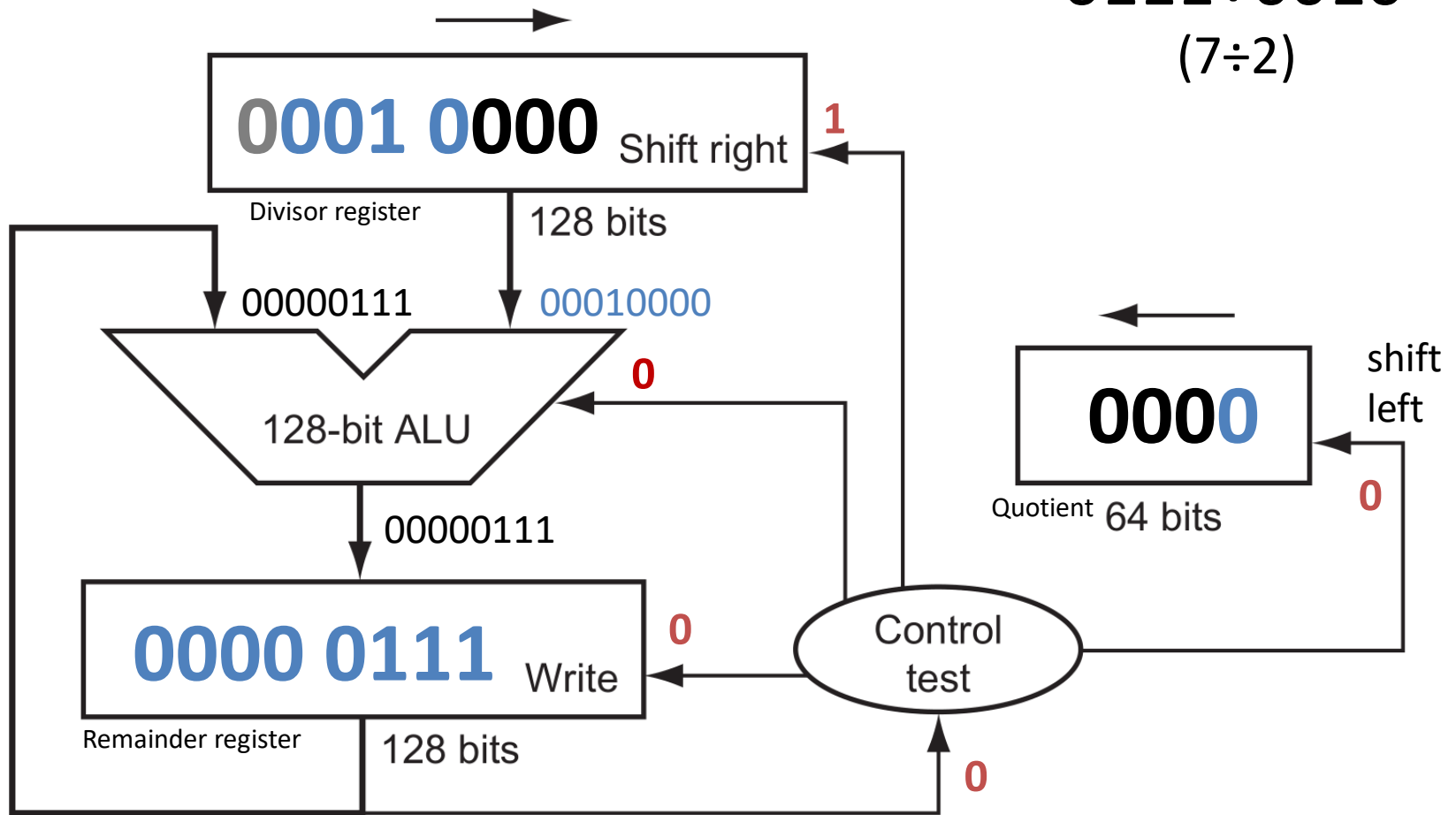

Division Example $7 \div 2$ ($0111 \div 0010$)

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: $\text{Rem} = \text{Rem} - \text{Div}$	0000	0010 0000	①110 0111
	2b: $\text{Rem} < 0 \Rightarrow +\text{Div}, \text{sll } Q, Q_0 = 0$	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: $\text{Rem} = \text{Rem} - \text{Div}$	0000	0001 0000	①111 0111
	2b: $\text{Rem} < 0 \Rightarrow +\text{Div}, \text{sll } Q, Q_0 = 0$	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: $\text{Rem} = \text{Rem} - \text{Div}$	0000	0000 1000	①111 1111
	2b: $\text{Rem} < 0 \Rightarrow +\text{Div}, \text{sll } Q, Q_0 = 0$	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: $\text{Rem} = \text{Rem} - \text{Div}$	0000	0000 0100	①000 0011
	2a: $\text{Rem} \geq 0 \Rightarrow \text{sll } Q, Q_0 = 1$	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: $\text{Rem} = \text{Rem} - \text{Div}$	0001	0000 0010	①000 0001
	2a: $\text{Rem} \geq 0 \Rightarrow \text{sll } Q, Q_0 = 1$	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001


Improved Division Hardware

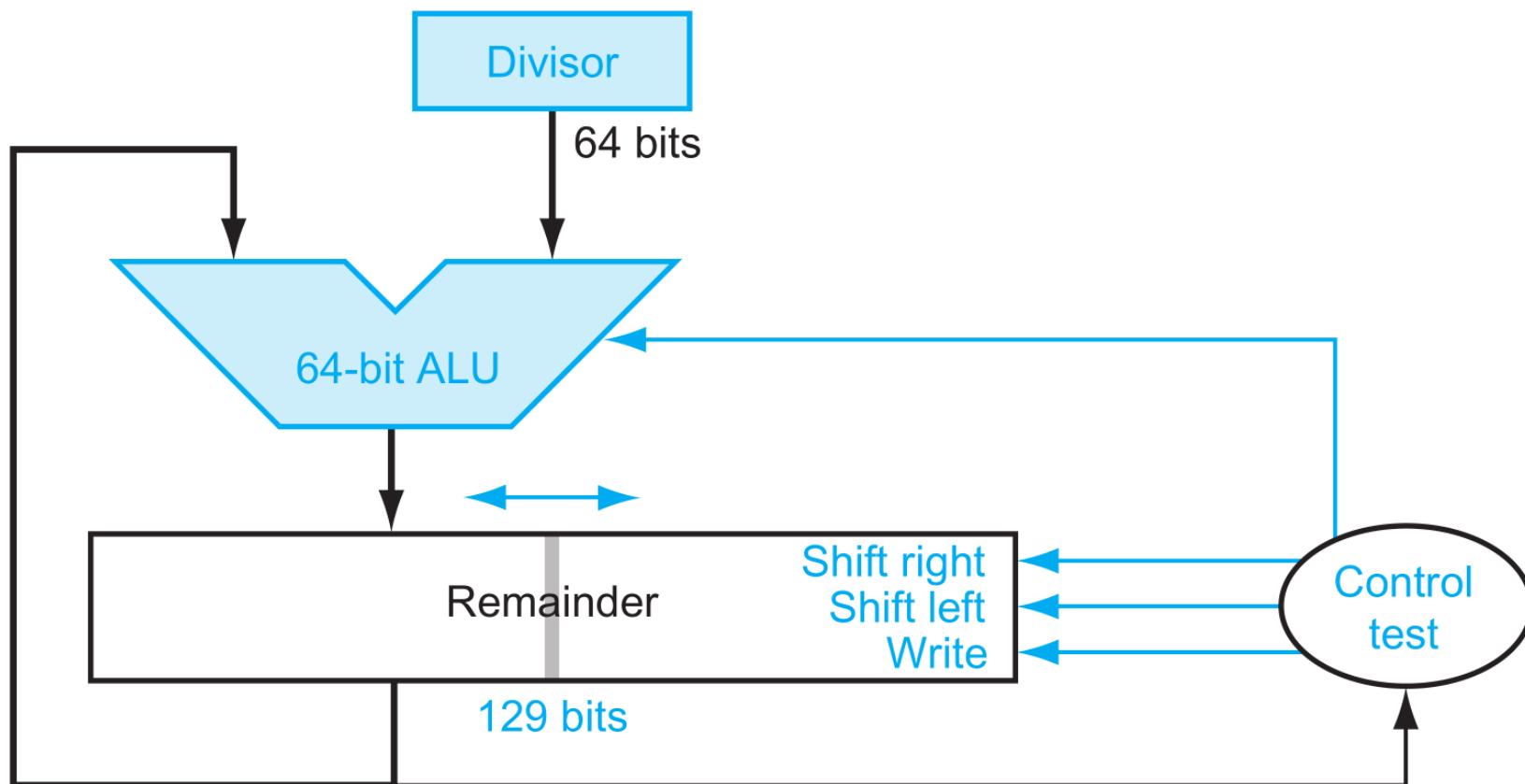

Improved Division Hardware

Iteration 0


Setting up registers

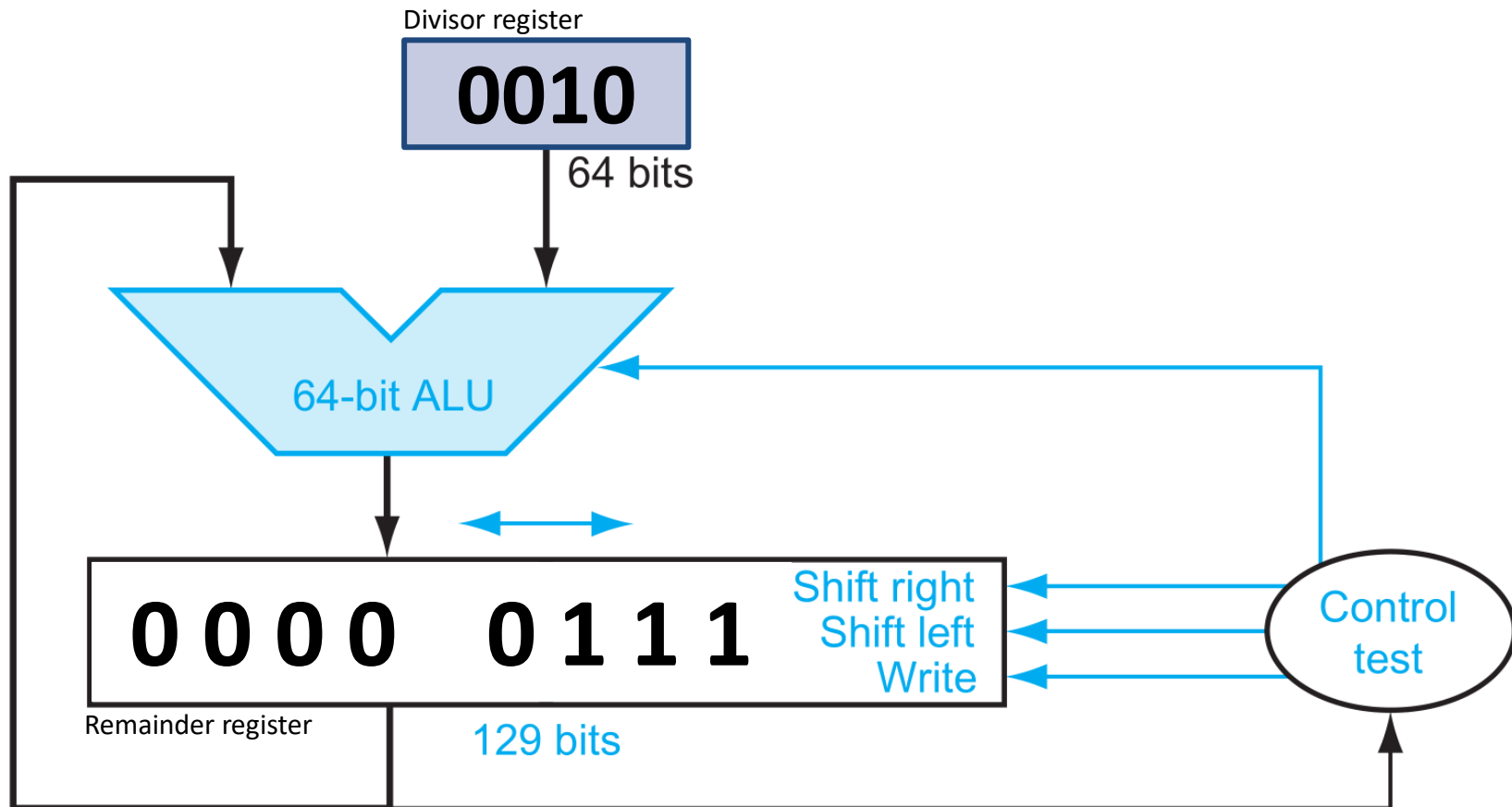

Improved Division Hardware

Iteration 1

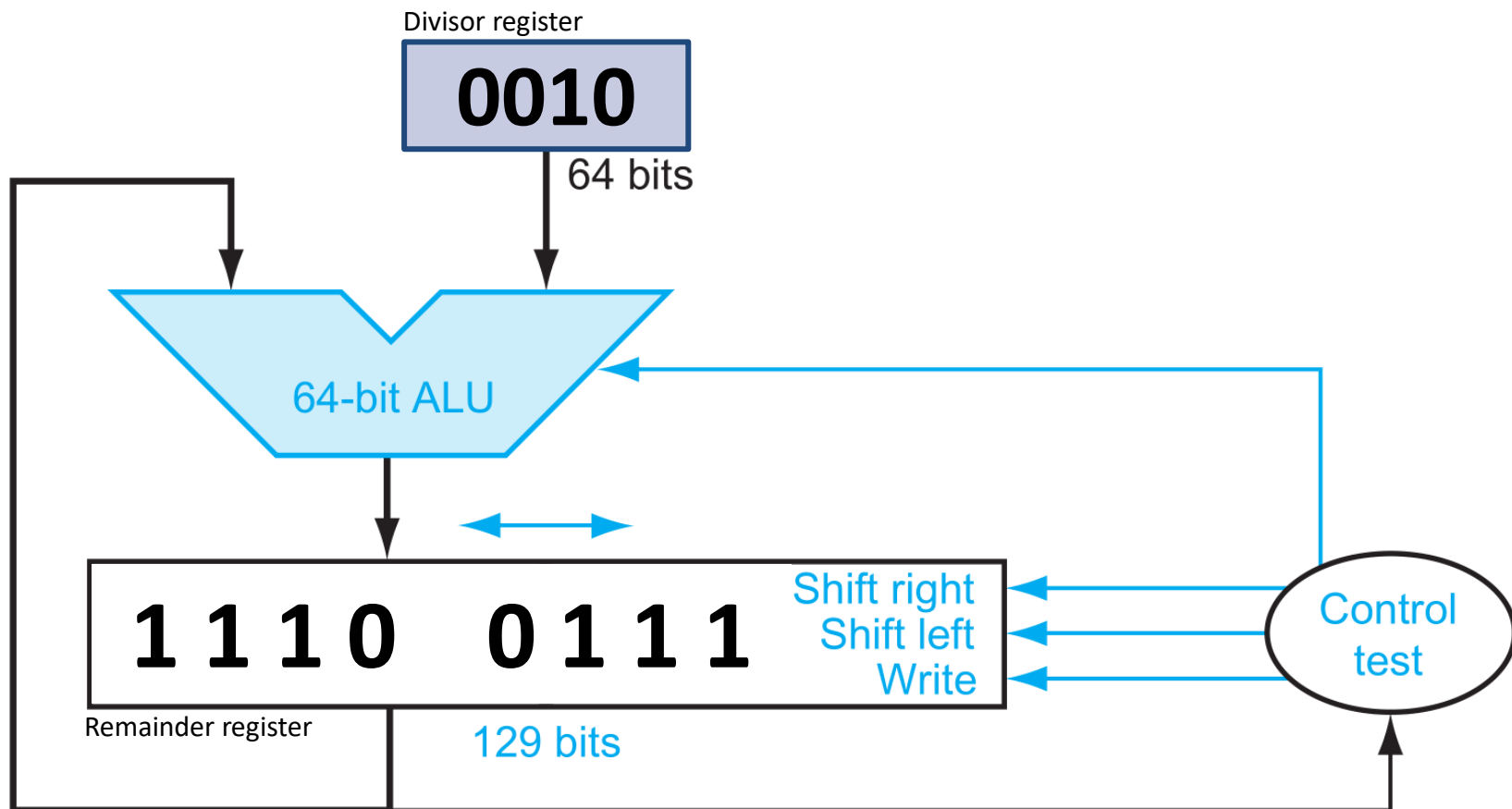
Left of the remainder = Left of the remainder - divisor



Improved Division Hardware

Iteration 1


Test MSB to check if it is 1

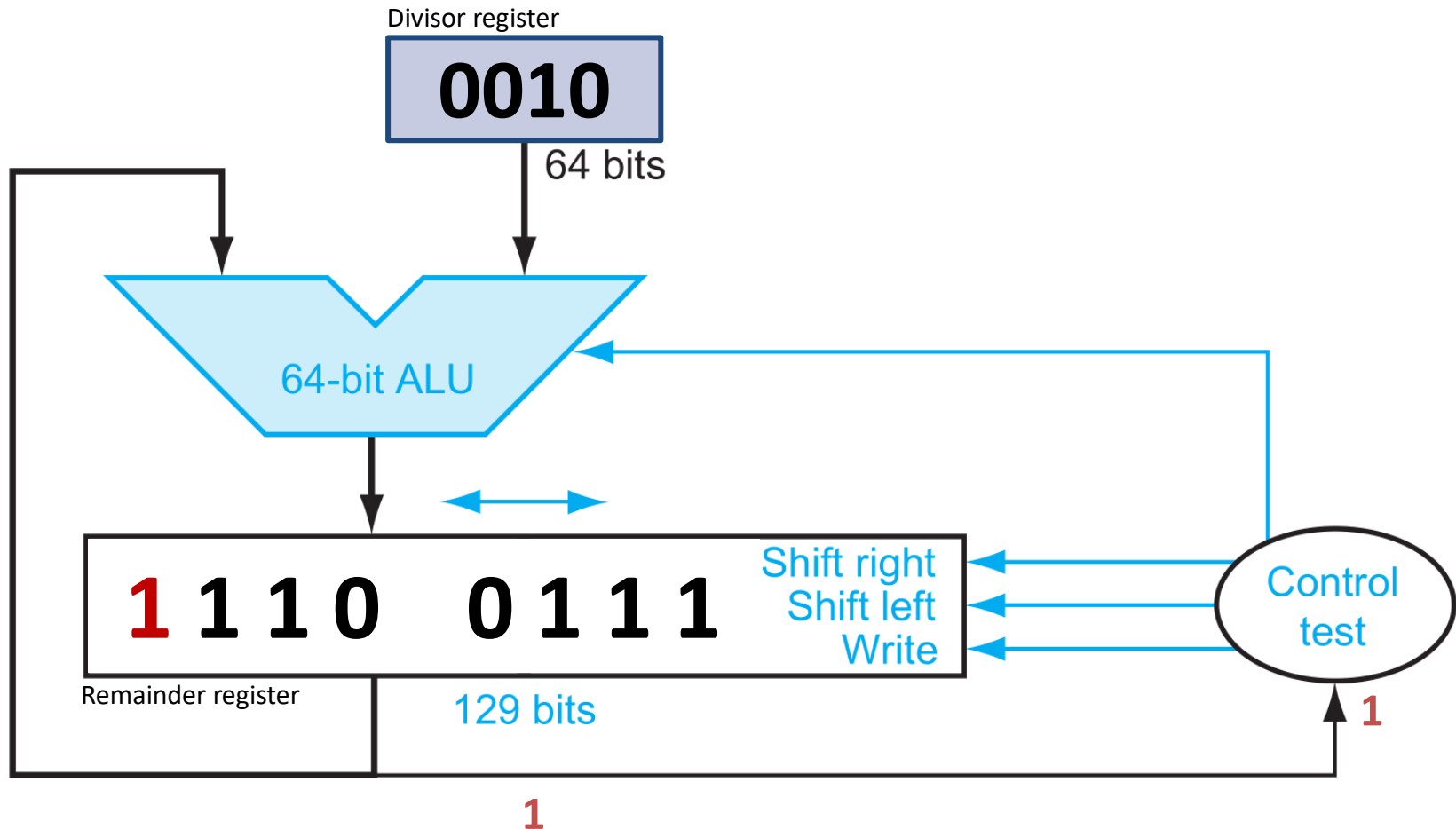

Improved Division Hardware

Iteration 1

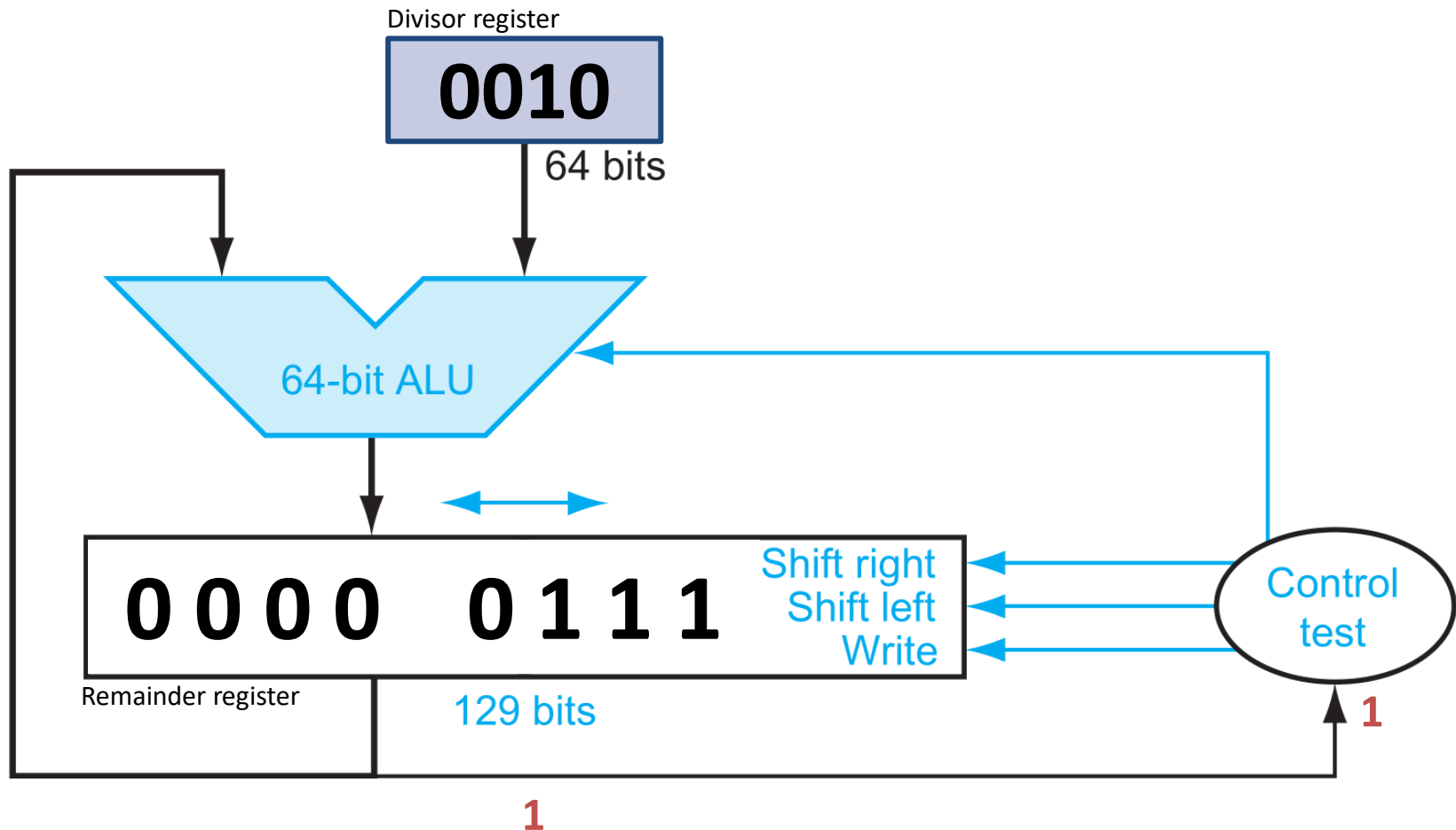
Restore by adding the divisor back to the remainder



Improved Division Hardware

Iteration 1


Shift left the remainder

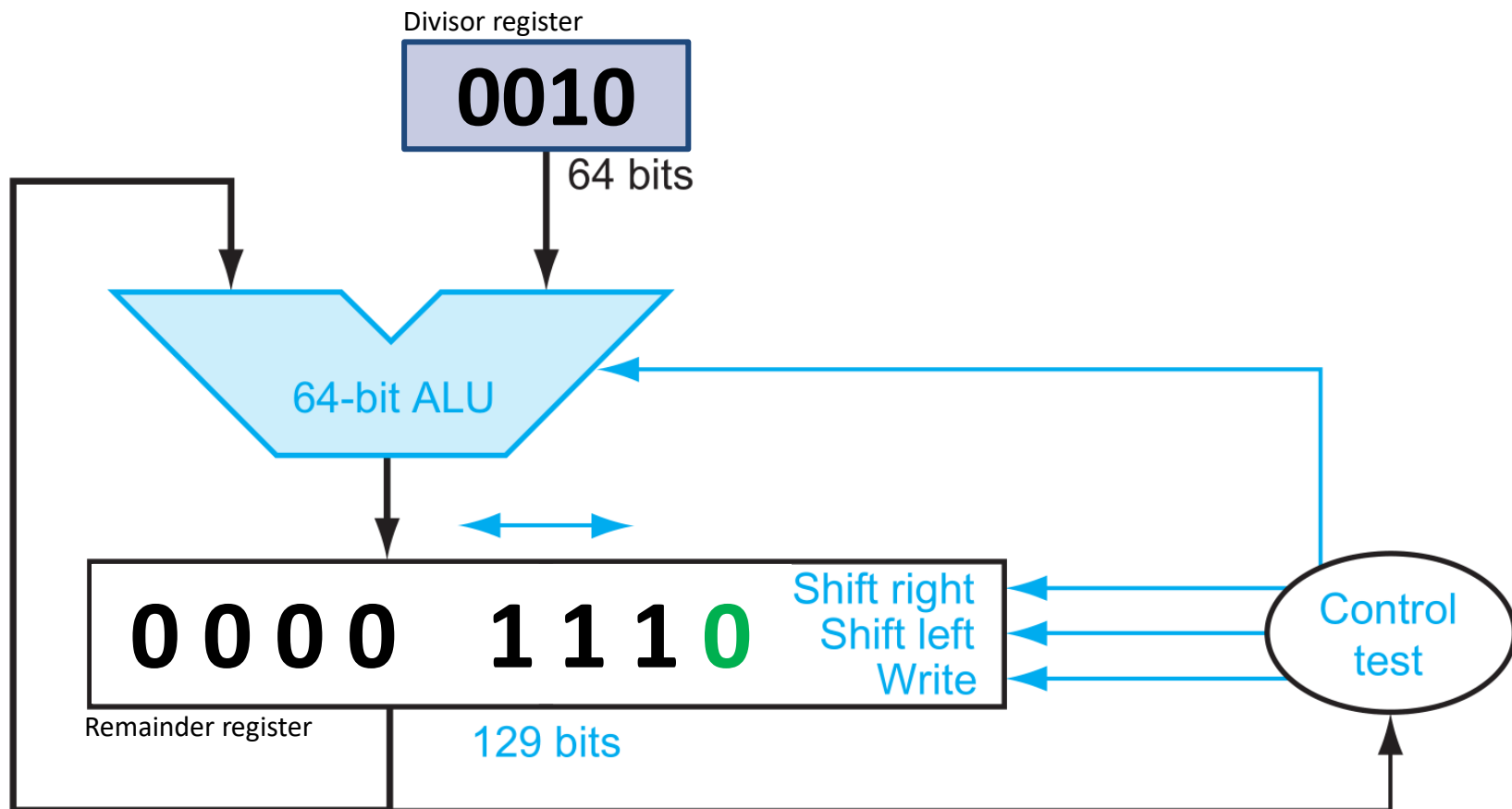

Improved Division Hardware

Iteration 2

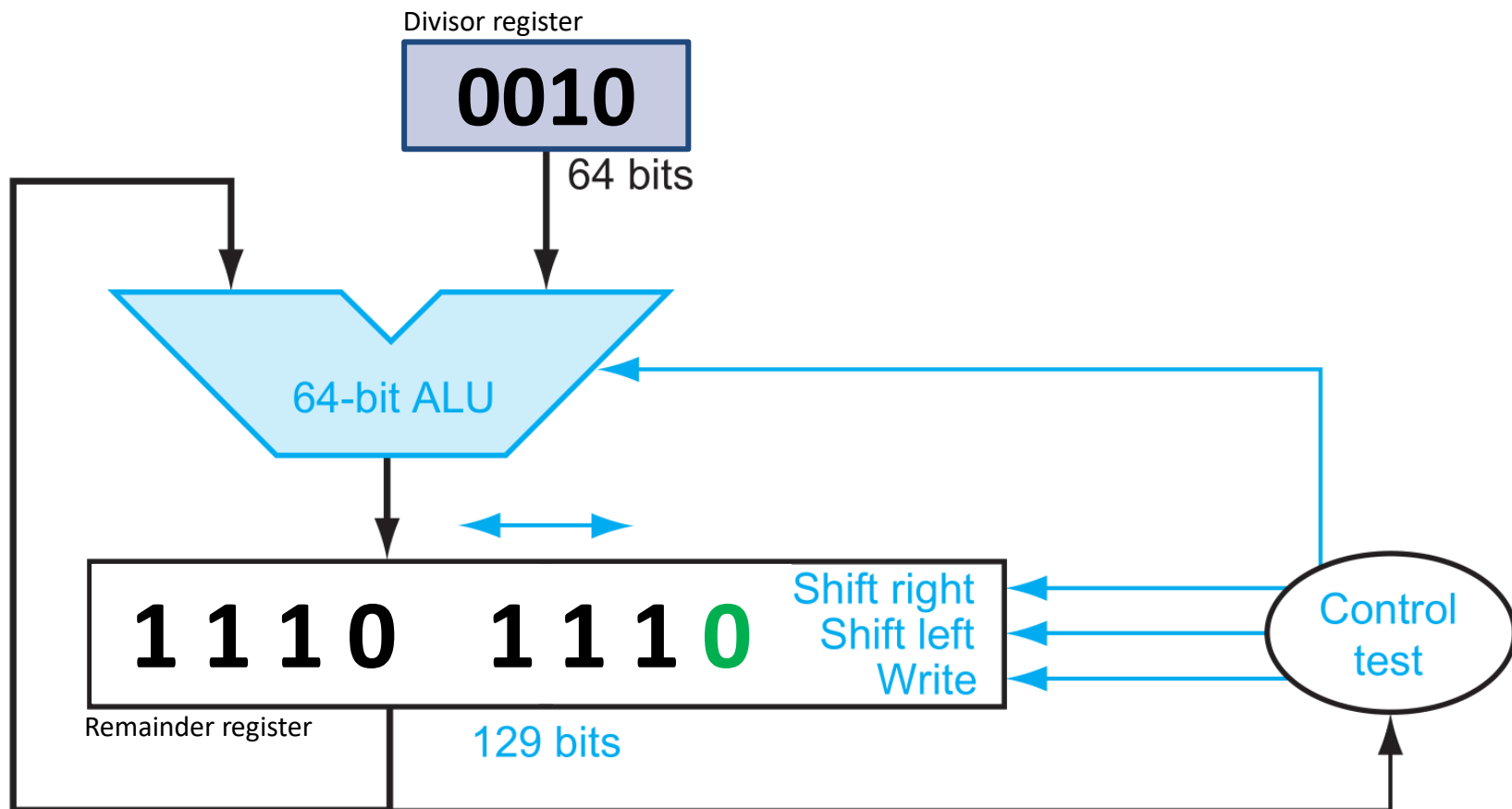
Left of the remainder = Left of the remainder - divisor



Improved Division Hardware

Iteration 2


Test MSB to check if it is 1

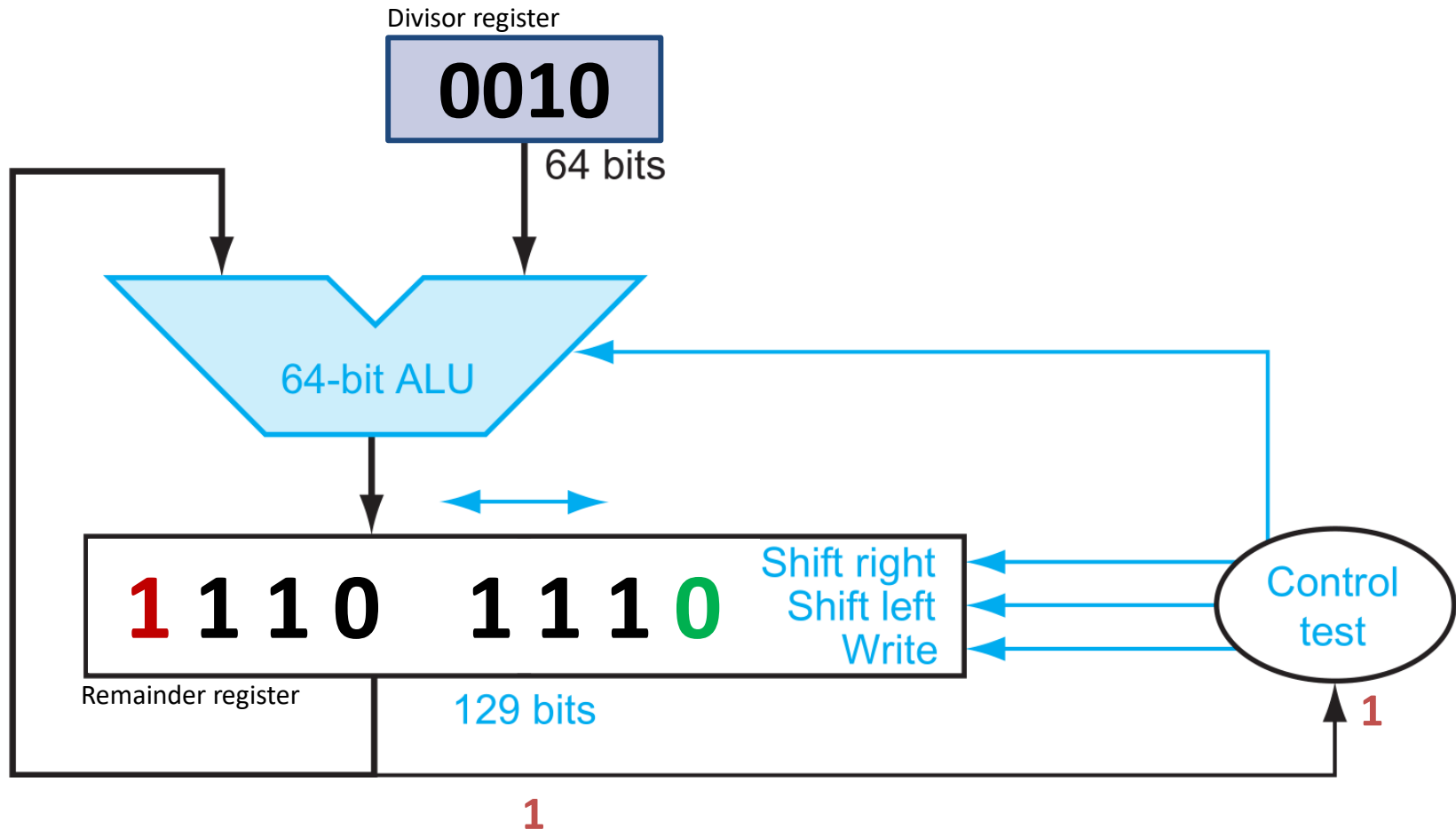

Improved Division Hardware

Iteration 2

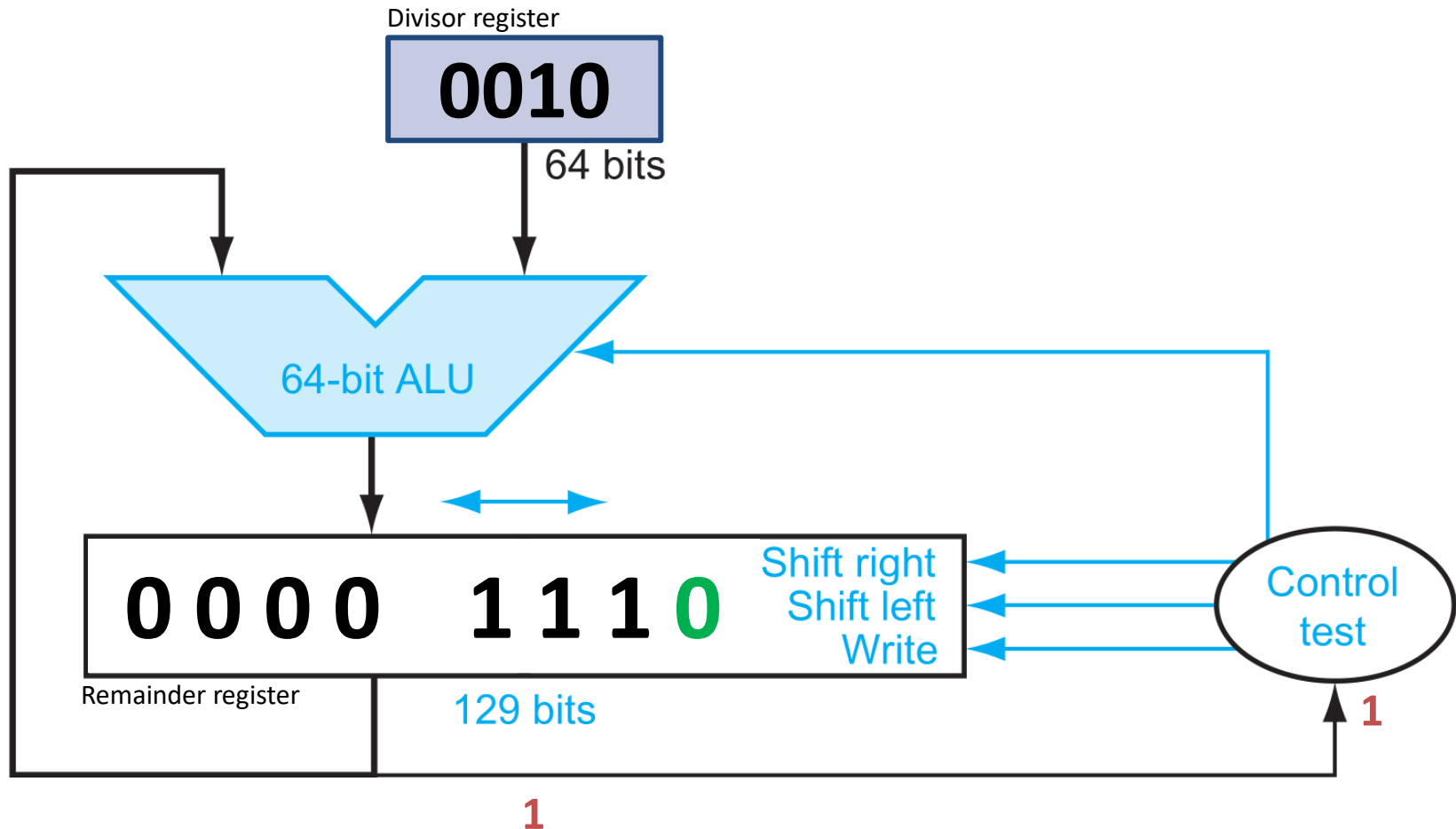
Restore by adding the divisor back to the remainder



Improved Division Hardware

Iteration 2


Shift left the remainder

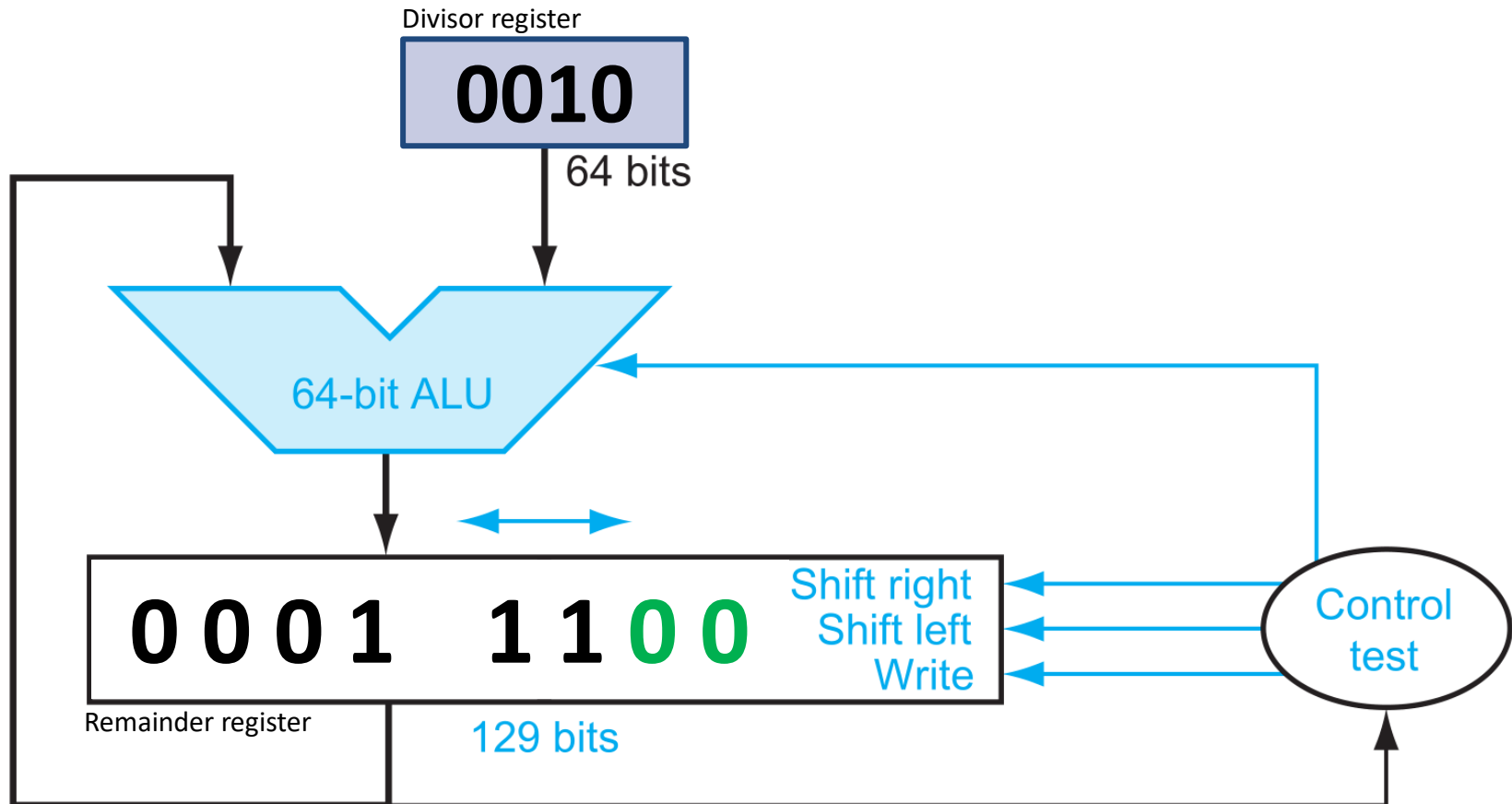

Improved Division Hardware

Iteration 3

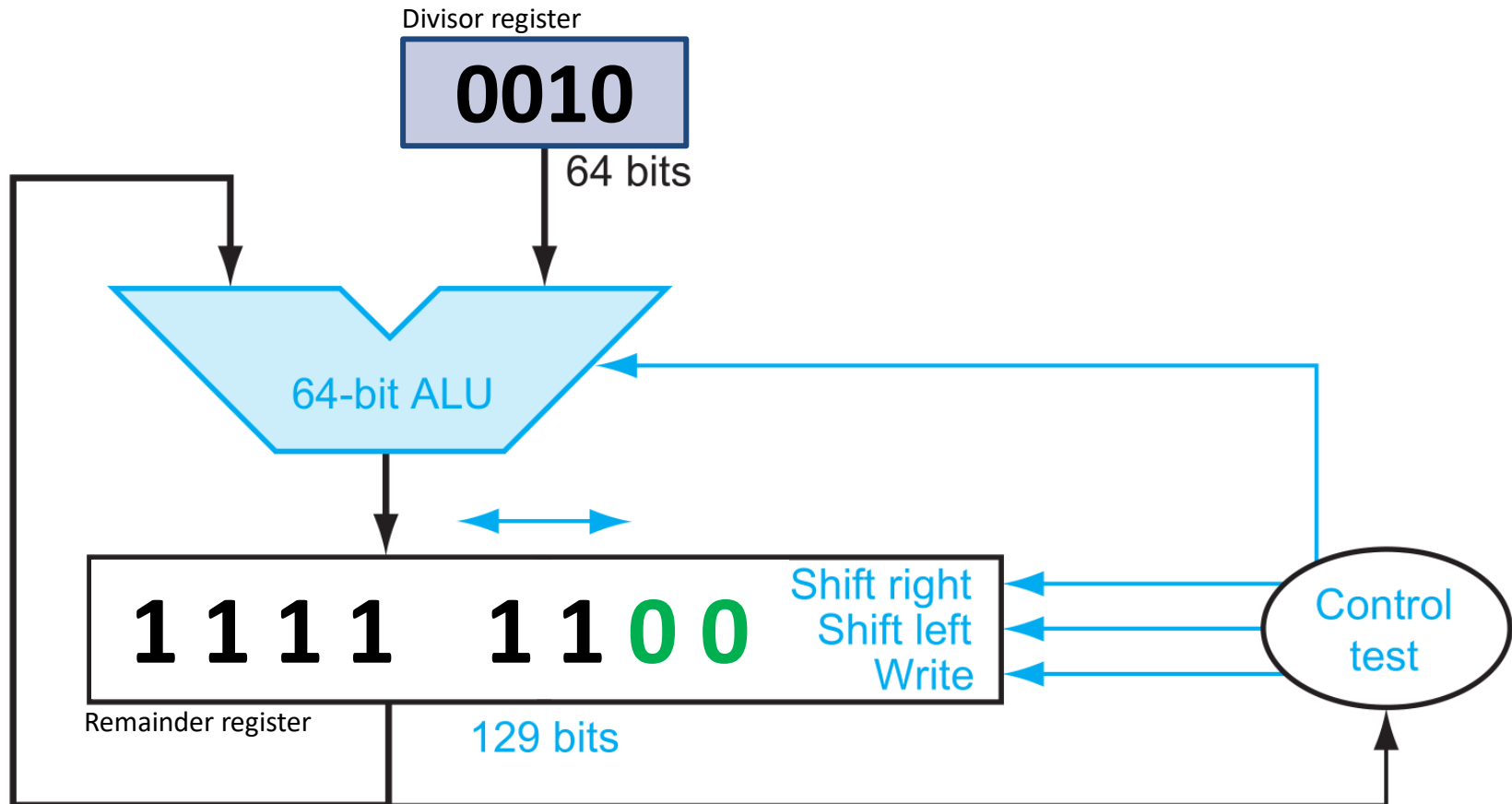
Left of the remainder = Left of the remainder - divisor



Improved Division Hardware

Iteration 3


Test MSB to check if it is 1

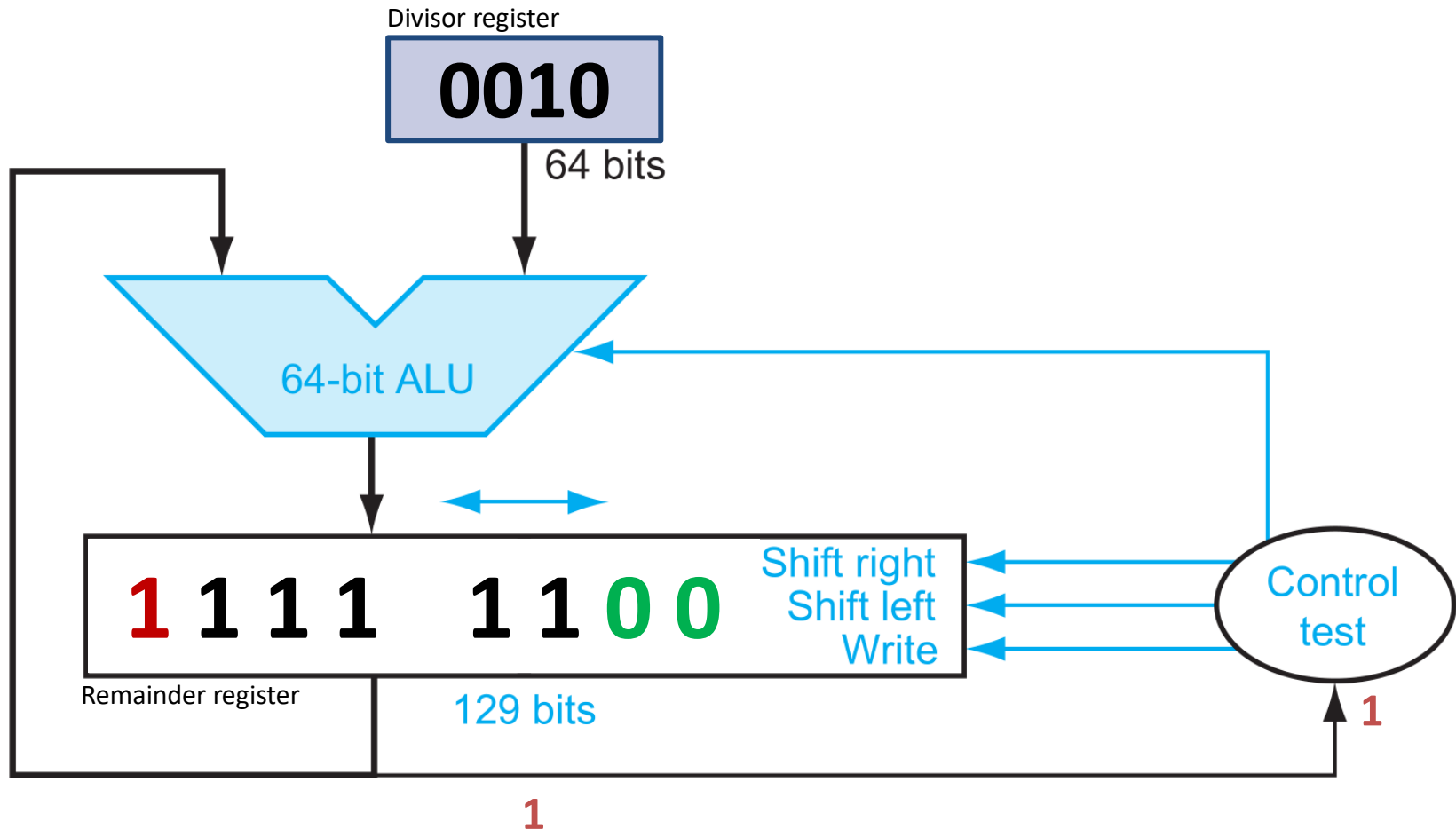

Improved Division Hardware

Iteration 3

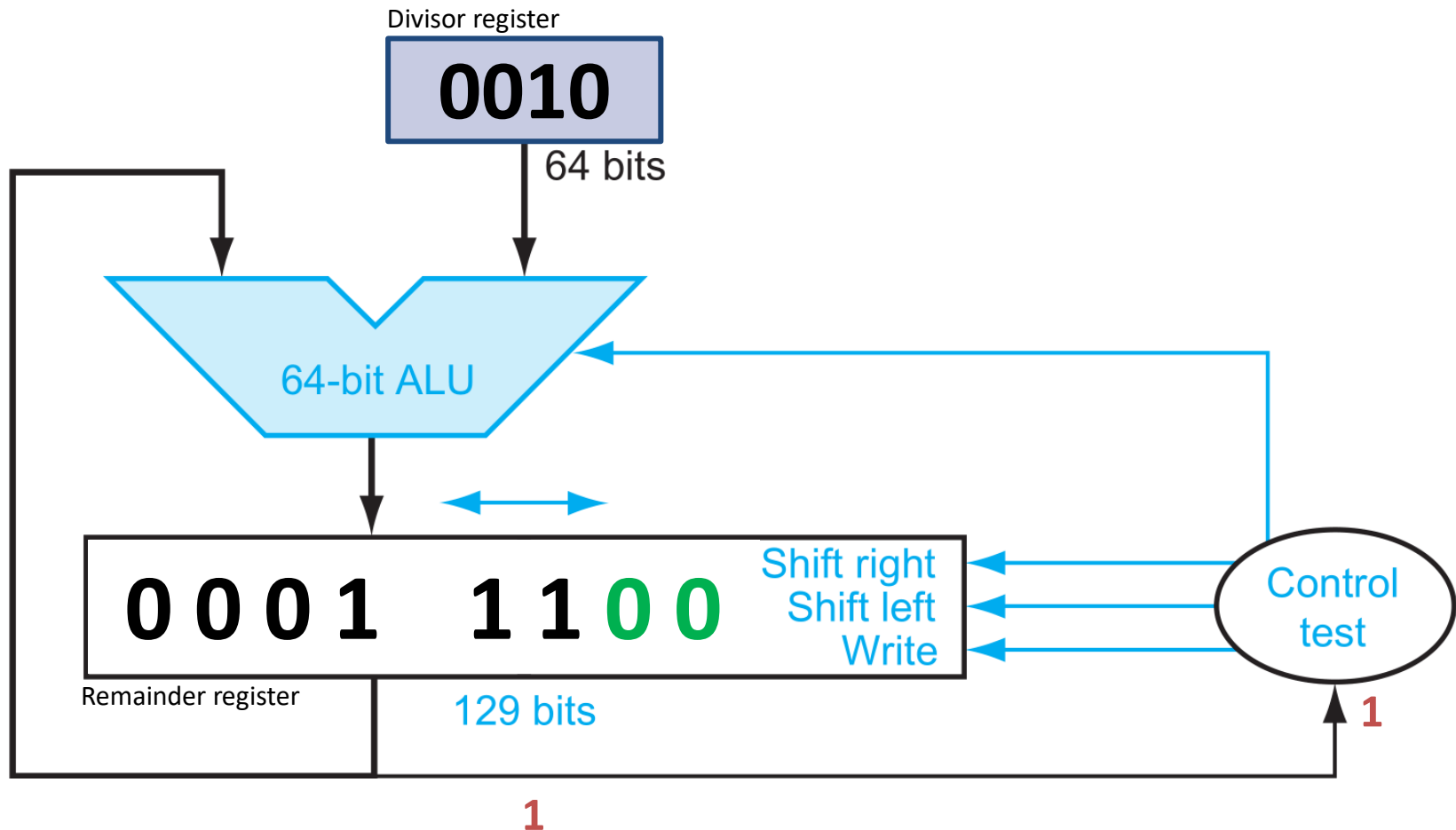
Restore by adding the divisor back to the remainder



Improved Division Hardware

Iteration 3


Shift left the remainder

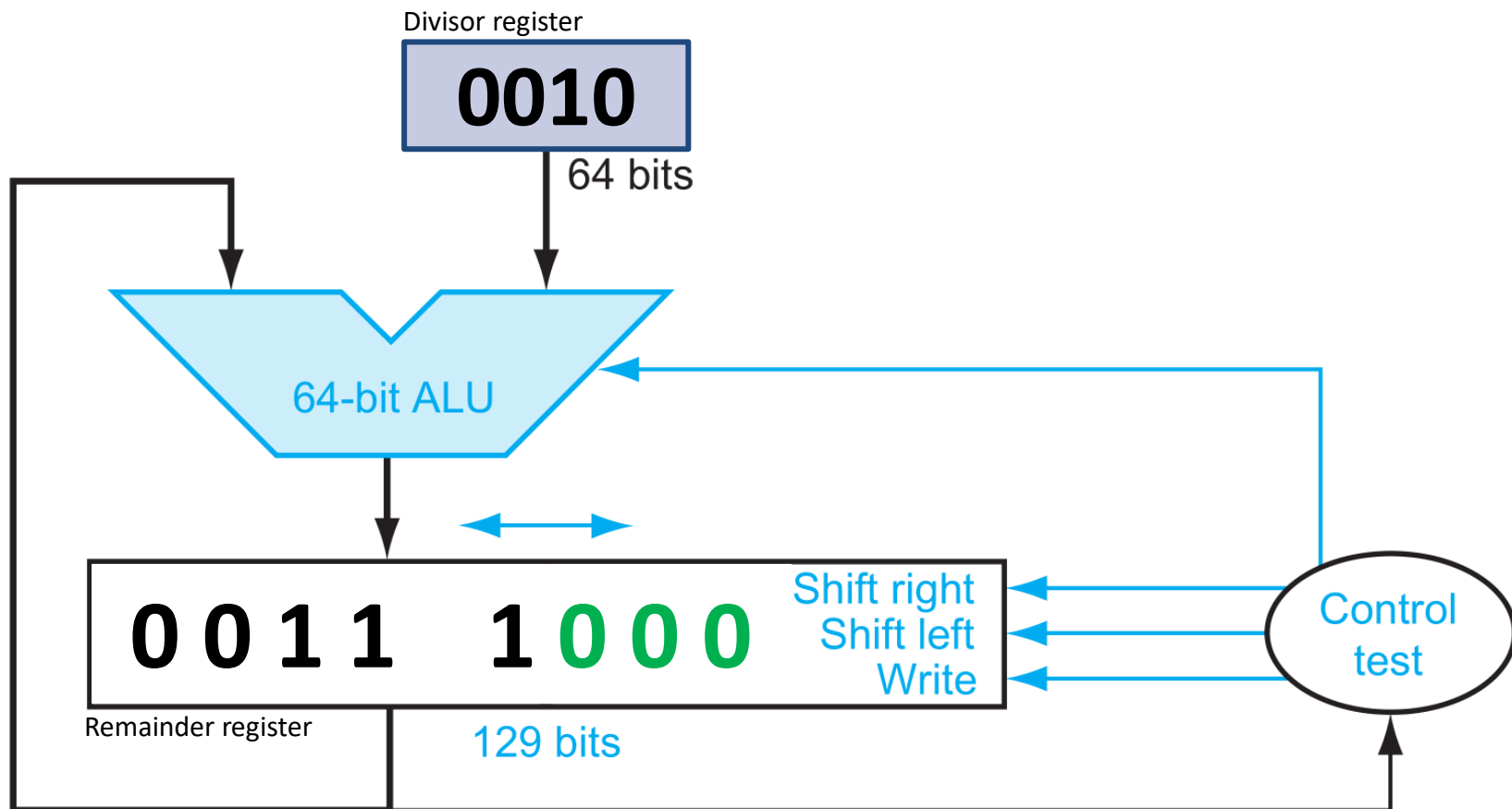

Improved Division Hardware

Iteration 4

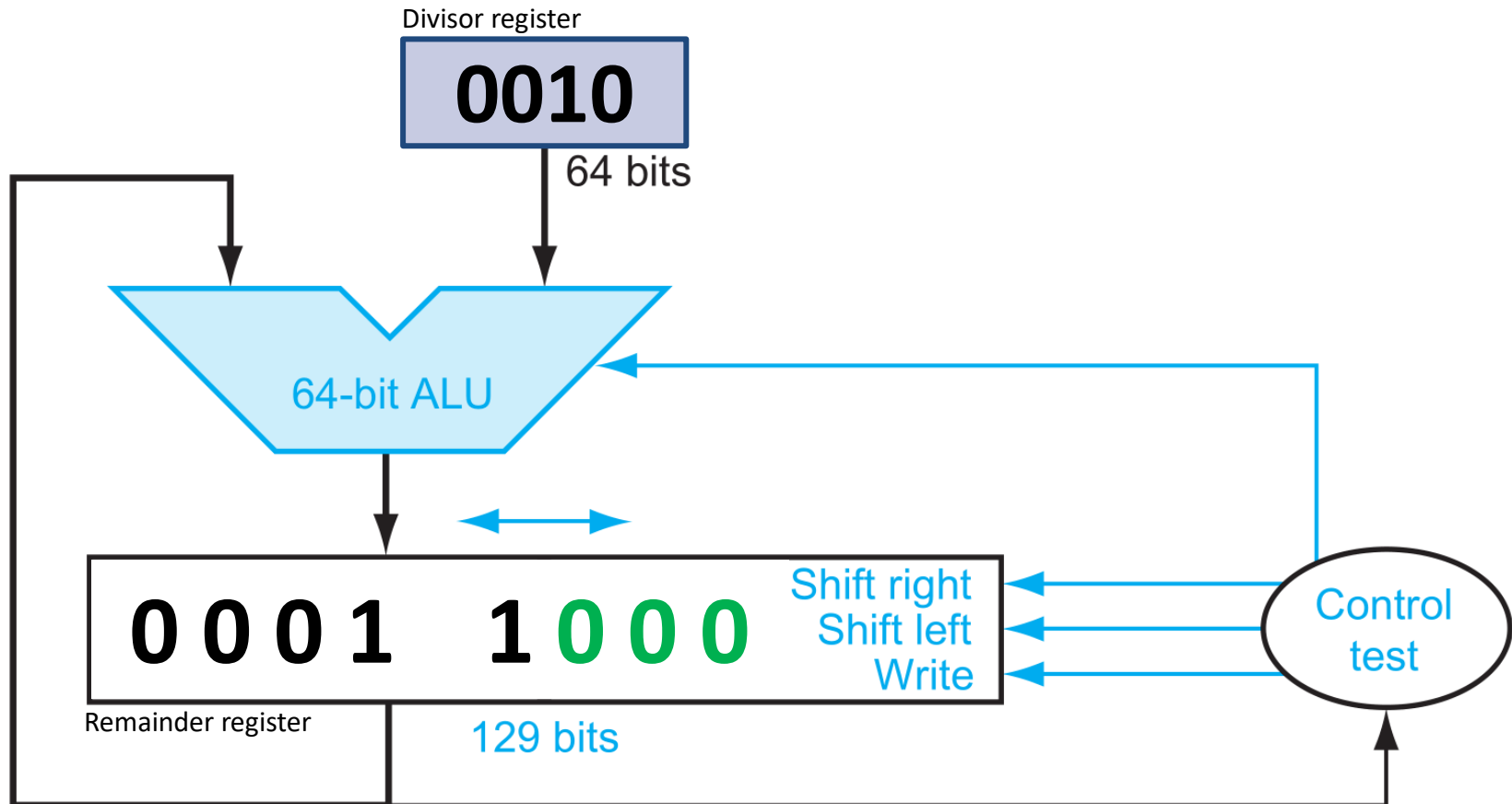
Left of the remainder = Left of the remainder - divisor



Improved Division Hardware

Iteration 4


Test MSB to check if it is 1

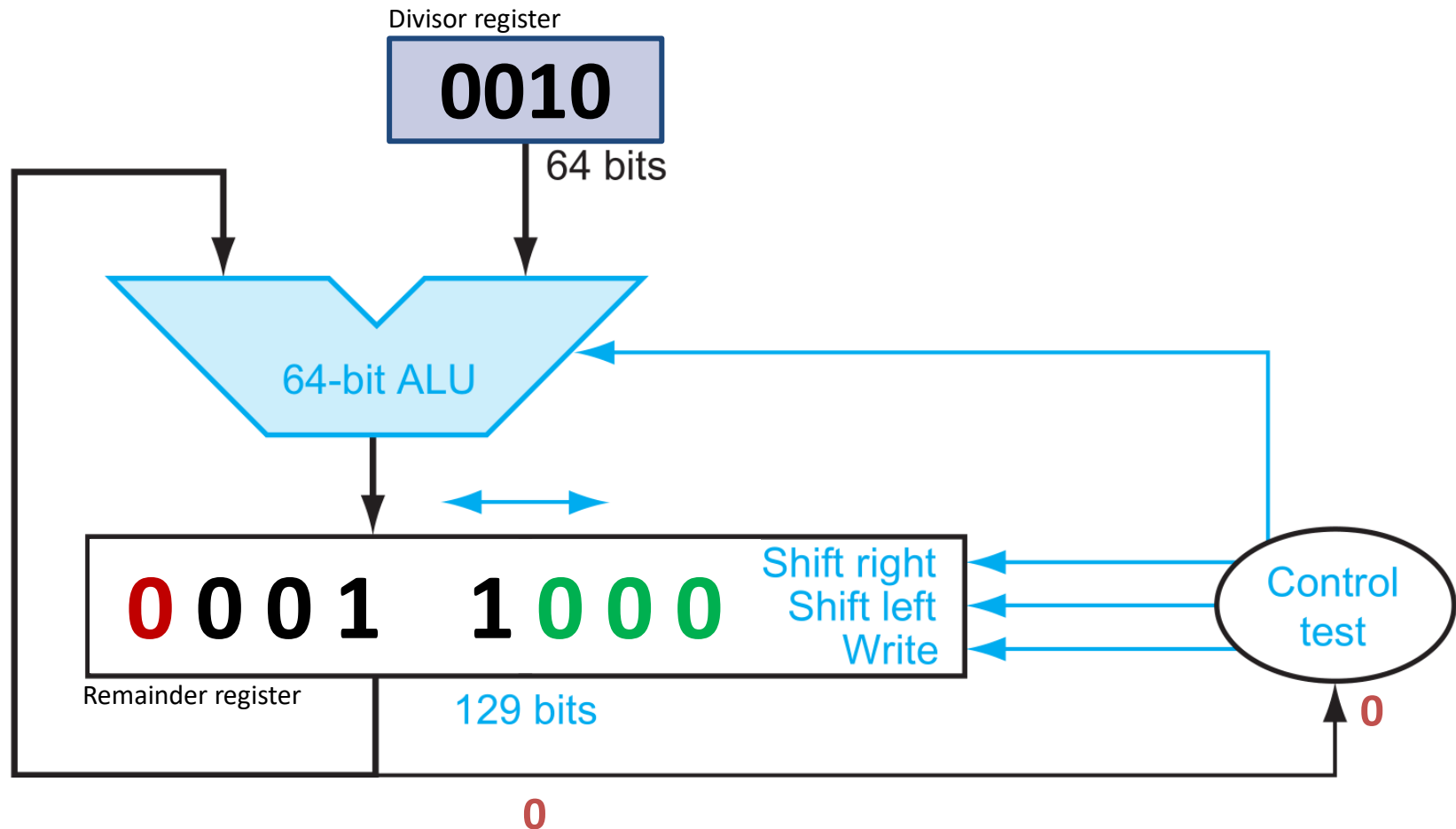

Improved Division Hardware

Iteration 4


Shift left the remainder

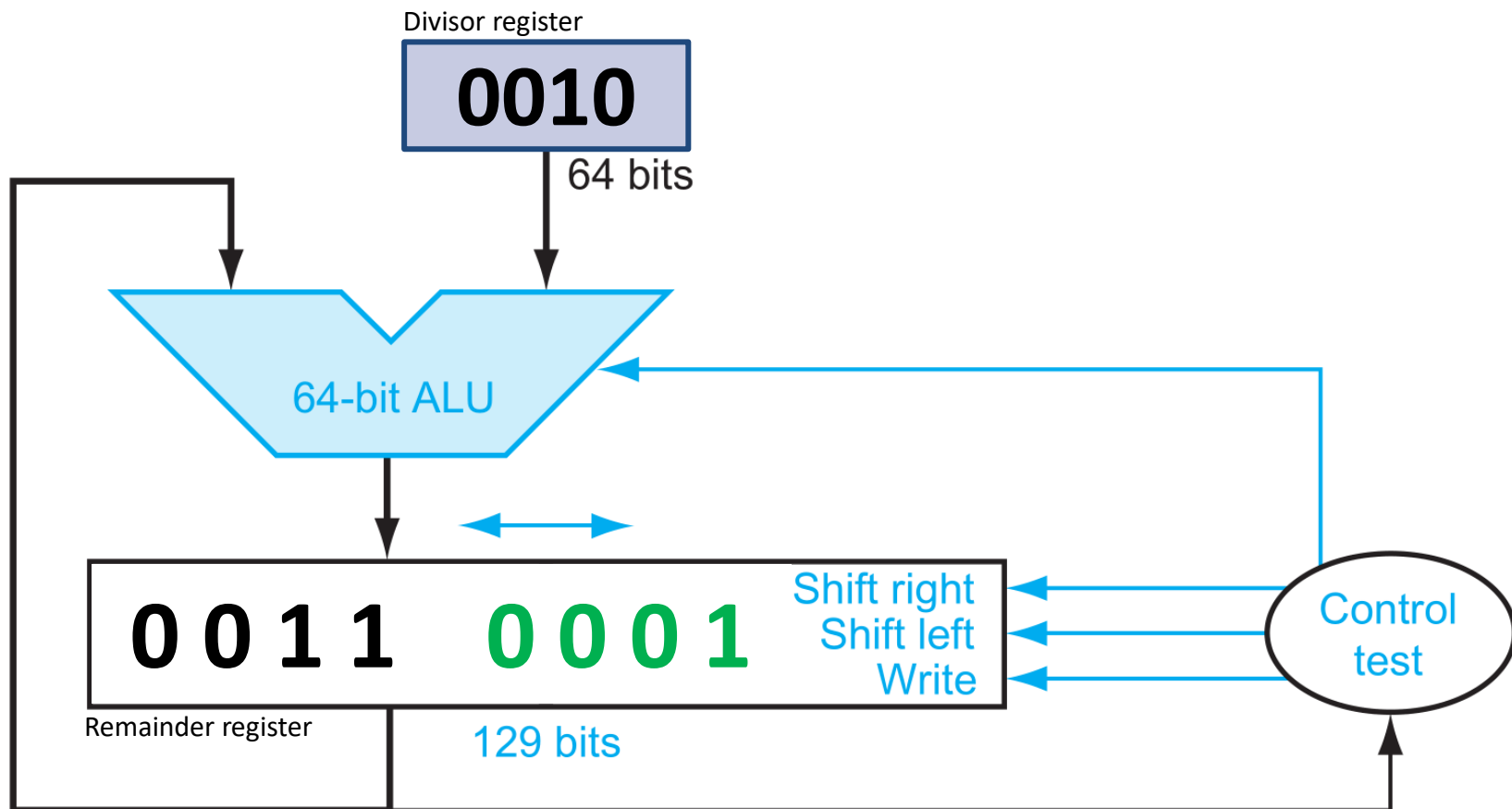

Improved Division Hardware

Iteration 5

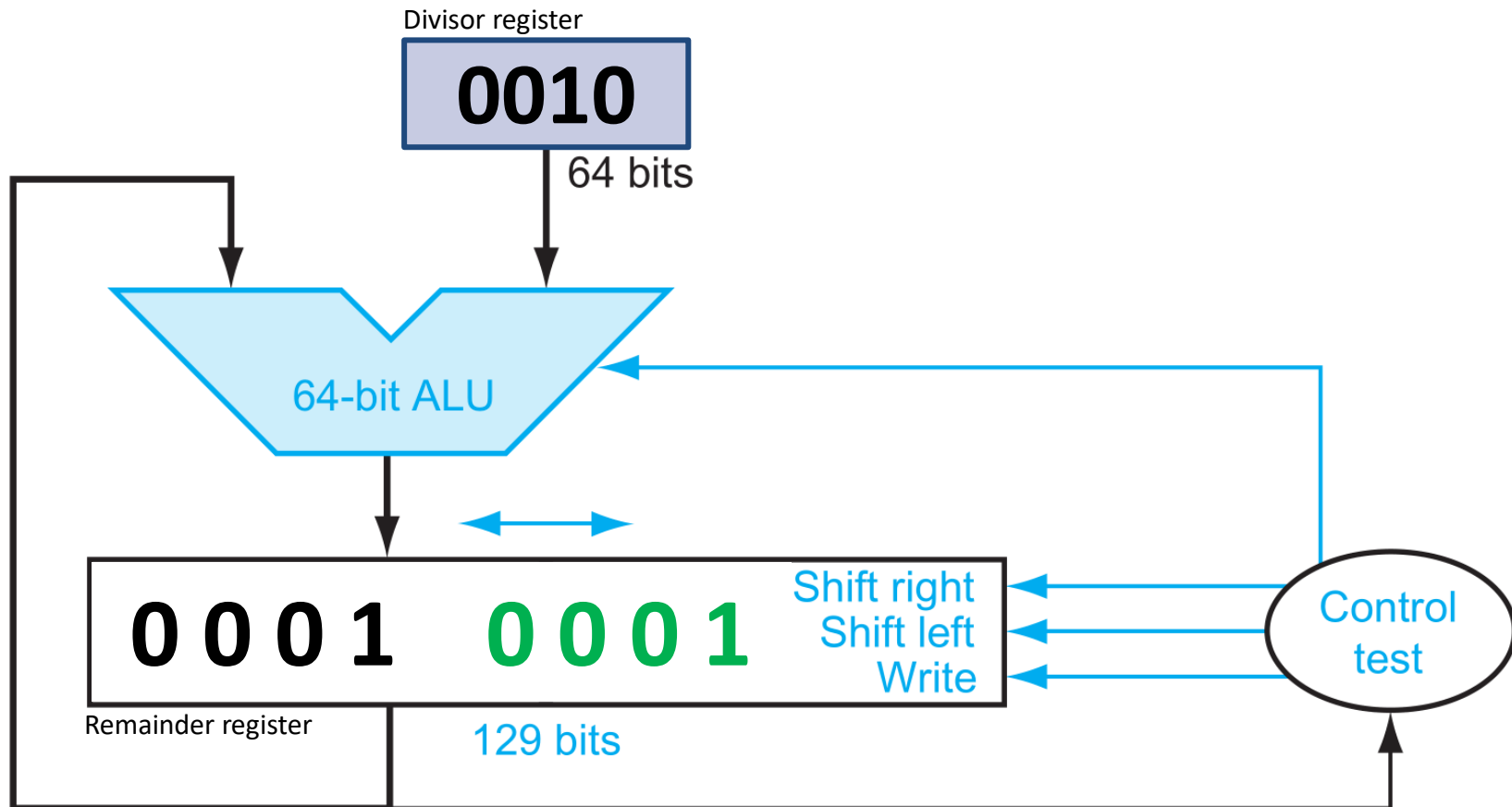
Left of the remainder = Left of the remainder - divisor



Improved Division Hardware

Iteration 5


Test MSB to check if it is 1

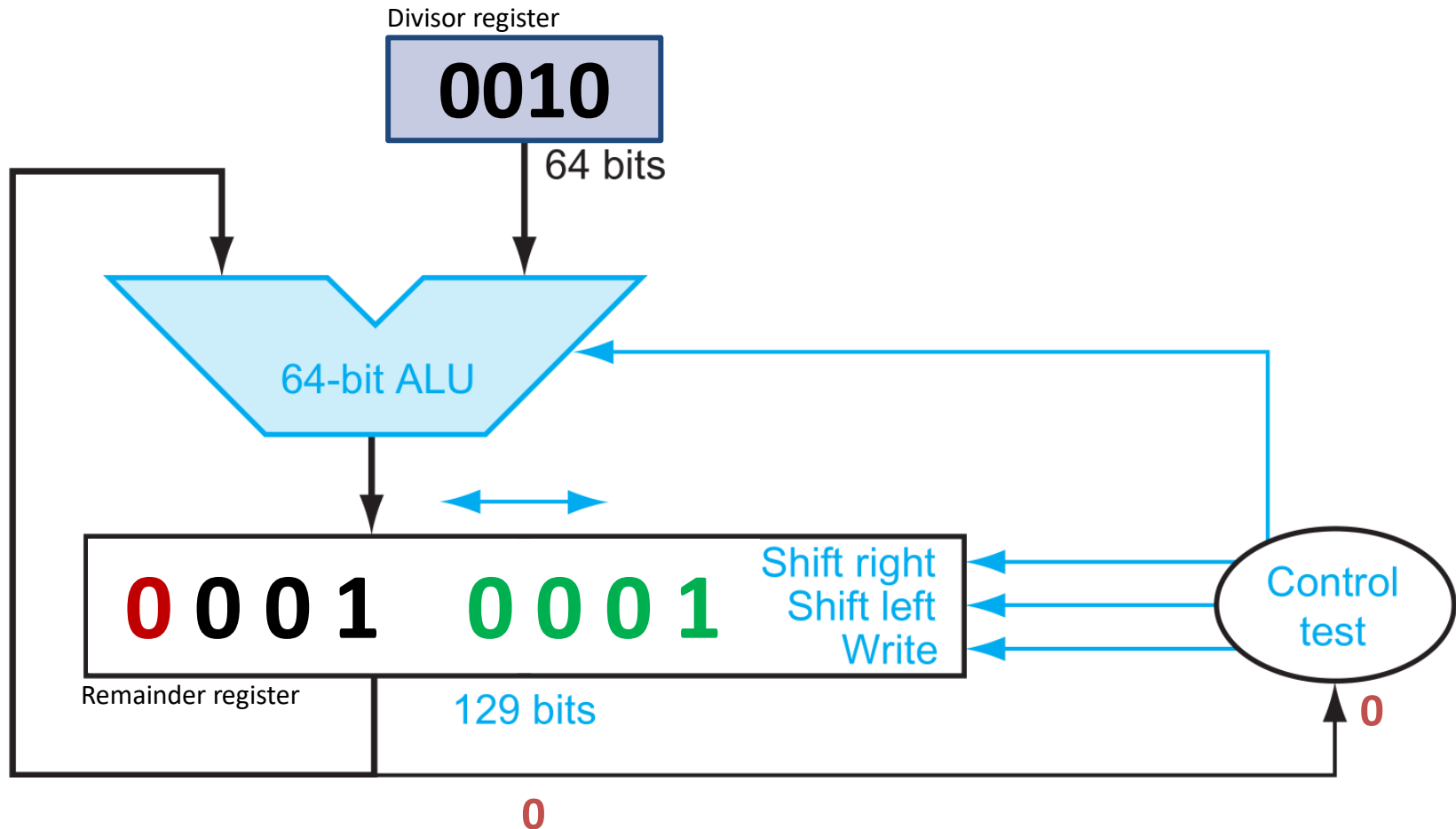

Improved Division Hardware

Iteration 5


Shift left the remainder

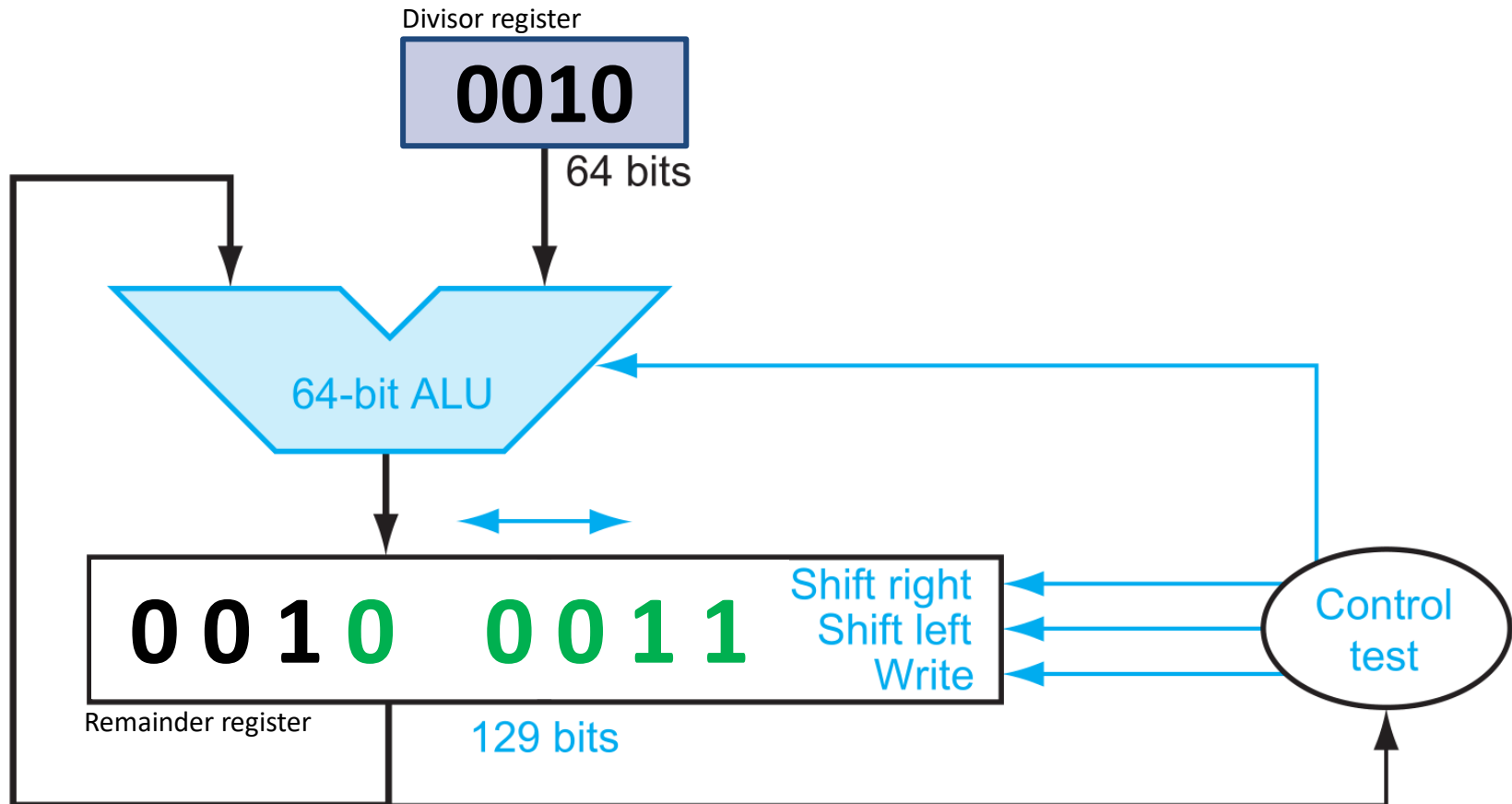

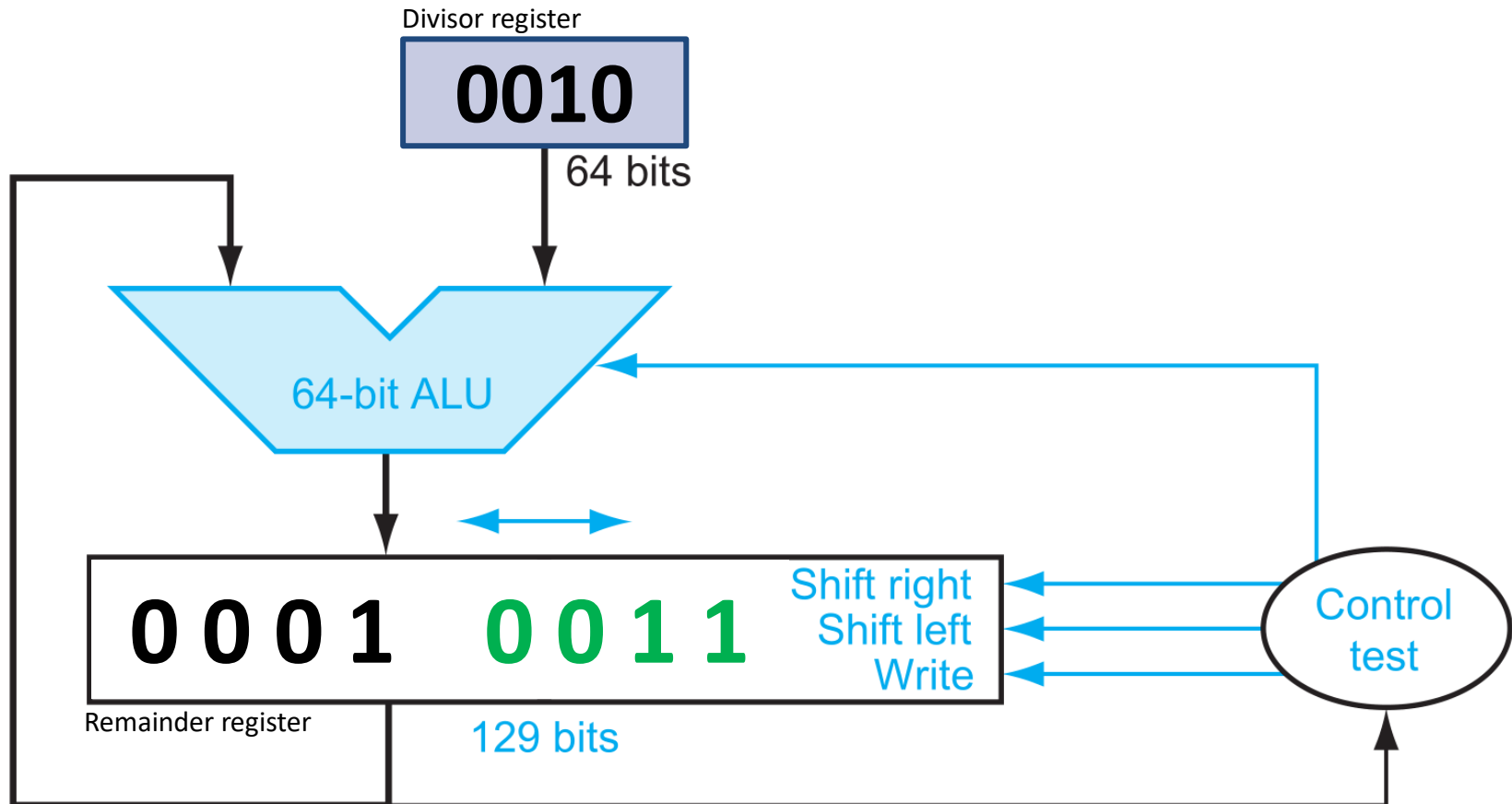
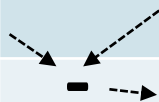



Improved Division Hardware

Last Adjustment

Shift right the left-half of the remainder



Improved Division HW

Iteration	Step	Divisor	Remainder (Quotient will place in right half)
0	Initial Values	0010	0000 : 0111
1	1: Rem = Rem - Div	0010	 1 110 : 0111
	2: Rem < 0 \rightarrow + Div, sll Q, Q0=0	0010	0000 : 1110 restore
2	1: Rem = Rem - Div	0010	 1 110 : 1110
	2: Rem < 0 \rightarrow + Div, sll Q, Q0=0	0010	0001 : 1100 restore
3	1: Rem = Rem - Div	0010	 1 111 : 1100
	2: Rem < 0 \rightarrow + Div, sll Q, Q0=0	0010	0011 : 1000 restore
4	1: Rem = Rem - Div	0010	 0 001 : 1000
	2: Rem >= 0 \rightarrow sll Q, Q0=1	0010	0011 : 0001
5	1: Rem = Rem - Div	0010	 0 001 : 0001
	2: Rem >= 0 \rightarrow sll Q, Q0=1	0010	0010 : 0011
6	Shift right the left half of remainder	0010	0001 : 0011

Improved Division Hardware

**need subtraction
capability**

32bit divisor subtracted
from left half of remainder

- Compare with mult H/W

